

1 01 0 1


Basic Electrical and Electronics Engineering

Electrical and Electronics Engineering

00 011

0101

1 1

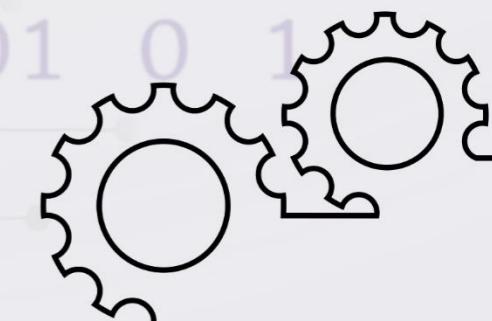









Topic No	Topic	Concept Map number
UNIT 1 ELECTRICAL CIRCUITS		
1	INTRODUCTION	1
	✓ Basic Terminologies	1
	✓ Types of Electrical Circuits	1
	✓ Classification of Electrical Network	1
	✓ 'V' and 'I' equation and Phasor relation of R,L,C	1
2	Ohm's Law, Kirchoffs Law	2
	✓ Kirchoff's Current Law	2
	✓ Kirchoff's Voltage Law	2
3	Source Transformation	2
4	Series and Parallel Circuits	3
	✓ Resistors in Series with Voltage Division Rule	3
	✓ Resistance in Parallel with Current Division Rule	3
	✓ Inductance in Series & Parallel	3
	✓ Capacitance in Series & Parallel	3
	✓ Problems	3
5	Mesh and Nodal Analysis - DC Circuits	4
	✓ Steps for Mesh Current Analysis	4
	✓ Steps for Nodal Voltage Analysis	4
	✓ Problem on Mesh Current Analysis	4
	✓ Problem on Nodal Voltage Analysis	4
6	Mesh and Nodal Analysis - AC Circuits	5
	✓ Problem on Mesh Current Analysis	5
	✓ Problem on Nodal Voltage Analysis	5
7	Star Delta Transformation	6
	✓ Delta to Star Transformation	6
	✓ Star to Delta Transformation	6
	✓ Problems	6
8	Alternating Circuit (AC) Fundamentals	6
9	Definition: Form Factor, Peak Factor, RMS Value	7
10	Analysis of Steady-State AC Circuits	7
	✓ Complex notation	7
	✓ Phasor Diagram, Power & pf of R,L,C,RL,RC,RLC	7

UNIT 2 ELECTRICAL MACHINES AND TRANSFORMERS		
11	Lenz'law, Fleming's righr and Left hand Rule	8
12	DC Generator	8
	✓ Construction & Principle of Operation	8
13	Basic Equation & Applications of DC Generators	9
	✓ EMF Equation of DC Generator	9
	✓ Types of DC Generator	9
	✓ Separately Excited DC Generators	9
	✓ Self Excited DC Generators	9
	✓ DC Shunt Generator	9
	✓ DC Series Generator	9
	✓ DC Compound Generator - Long & Short Shunt	9
	✓ Applications of DC Generators	9
14	DC Motors	10
	✓ Principle of Operation	10
	✓ Torque Equation of DC Motor	10
	✓ Types of DC Motor	10
	✓ Self Excited DC Motor	10
	✓ DC Shunt Motor	10
	✓ DC Series Motor	10
	✓ DC Compound Motor - Long & Short Shunt	10
	✓ Applications of DC Motor	10
15	Need of Starters and its Types	11
	✓ Need of Starters	11
	✓ Types of DC Motor Starters	11
	✓ Two point Starter	11
	✓ Three Point Starter	11
	✓ Four Point Starter	11
16	Faraday's Law of Electromagnetic Induction	12
17	Single Phase Transformers: Principle of Operation	12
18	EMF Equation of Transformer	12
UNIT 3 SEMICONDUCTOR DEVICES		
19	PN Diode - Operation & Characteristics	13
20	Zener Diode - Circuit & Characteristics	13
21	Photo Diodes - Circuit & Characteristics	13
22	Bipolar Junction Transistor	14
	✓ Circuit representation & Symbol	14
	✓ Operation of PNP & NPN transistor	14
	✓ CB Configuration: Input & Output Characteristics	14
23	Common Emitter Configuration	15
	✓ Input & Output Characteristics	15
24	Common Collector Configuration	15
	✓ Input & Output Characteristics	15
25	Operational Amplifiers	16
	✓ Inverting & Non-Inverting Amplifier	16
26	Applications of Semiconductor Devices	16
	✓ Application of PN Diode	16
	✓ Application of Zener Diode	16
	✓ Application of BJT	16
	✓ Application of Op-amp	16
UNIT 4 DIGITAL ELECTRONICS		
27	Binary Number System	17
	✓ Conversion and Problems	17
28	Logic Gates	18
29	Boolean Algebra	19
	✓ Simplification of Boolean Function	19
	✓ Postulates and Theorem of Boolean Algebra	19
	✓ Sum of Product form	19
	✓ Product of Sum form	19
30	Karnaugh Map (K-Map)	19
	✓ Steps involved and Problems	19
31	Adders - Half and Full Adder	20
32	Registers - Shift Registers	20
	✓ Types of Shift Register - SISO,SIPO,PISO,PIPO	20
33	Flipflops	21
	✓ Combinational Circuit	21
	✓ Sequential Circuit	21
	✓ Types of Flipflops - SR,D,JK,T	21
	✓ Master Slave Flipflop	21
34	Counters	22
	✓ Types of Counter, Modulus of Counter	22
	✓ Asynchronous Up Counter (3 Bit)	22
	✓ Asynchronous Down Counter (3 Bit)	22
	✓ Asynchronous Up/Down Counter	22
UNIT 5 ELECTRICAL INSTALLATION		
35	Domestic Wiring - Components and Types	23
36	Basic Principles of Earthing	23
37	Types of Batteries	24
	✓ Primary Batteries	24
	✓ Secondary Batteries	24
	✓ Important Characteristics for Batteries	24
38	General Safety requirement as per IE rules	25
39	Elementary Calculations for Energy Consumption	25
40	Power factor Improvement and Battery Backup	25
41	Application & Future Scope for Electrical & Electronics	26

EEAOI - ELECTRICAL CIRCUIT- INTRODUCTION

1

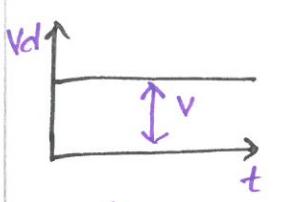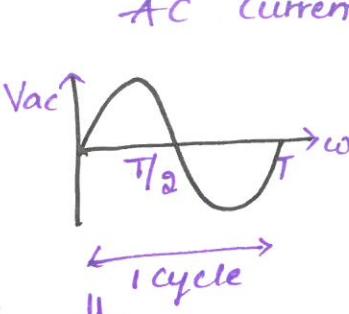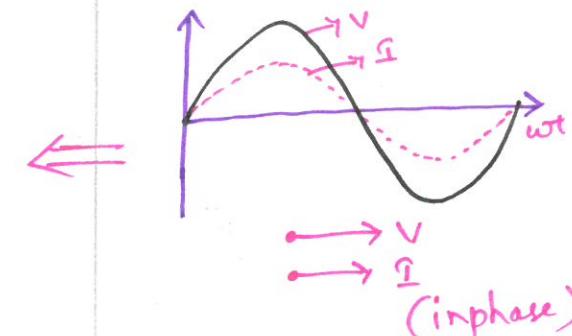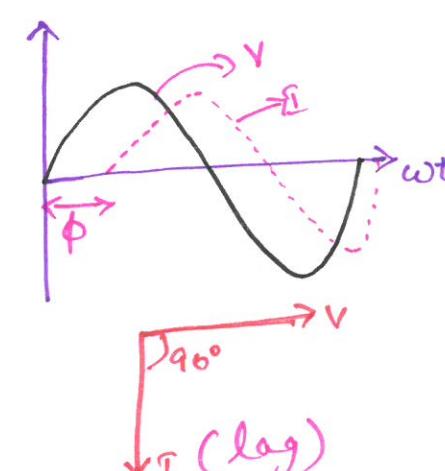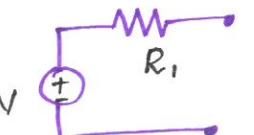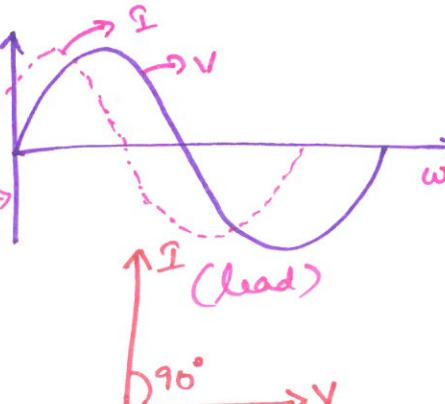	Basic Terminologies:	* DC current Has only magnitude	AC Current Has magnitude and frequency.	Element	VSI Equation	Phasor Relation.
* Charge (Q): Basic Quantity of Electric circuit	\rightarrow +ve or -ve charge \rightarrow unit columns			① Resistance : opposes the 'I' flow Symbol: R Unit = Ohms (Ω)	$VR = IR$ R (Ohm's law) $IR = \frac{VR}{R}$ $VR = V \angle 0^\circ$ $IR = I \angle 0^\circ$ $\phi = 0^\circ$ $Z = R + j0$	* Will not introduce any phase shift. 
* Current (I): flow of Electrons	\rightarrow unit : Amperes			Types of Electric Circuits: → closed circuit → open circuit $\rightarrow I=0$ → short circuit $\rightarrow V=0$ → Earth circuit		
* Voltage (V) = Potential difference between 2 points	\rightarrow unit : Volts	$V = \frac{\text{Workdone}}{\text{charge}} = \frac{W}{Q}$		Classification of Electrical Network (i) Active elements: Sources of Energy Passive Elements: R, L, C	$V = L \frac{di}{dt}$ $I = \frac{1}{L} \int i dt$	* Introduce 90° phase shift b/w V & I * 'I' lags 'V' by 90°
* Power (P): $V \times I$	or $P = \frac{\text{Energy}}{\text{Time}} = \frac{W}{t}$			(ii) Unilateral Elements: V, I relation is not same for both directions of Bilateral Elements: V, I relation is same.	$VL = V \angle 0^\circ$ $IL = I \angle -90^\circ$ $Z = R + jWL$ $= R + jXL$ $Z = 0 + jXL$	
* Network : Interconnection of 2 or more Elements				(iii) Linear Elements: obeys superposition Principle & Homogeneity. Non-linear Elements: Doesn't obey	$V = \frac{1}{C} \int i dt$ $i = C \frac{dv}{dt}$	* Introduce 90° phase shift b/w V & I . * 'I' leads 'V' by 90° .
* Circuit : Contains atleast one closed path				(iv) Lumped elements: physically separable . Ex: R, L, C .	$VC = V \angle 0^\circ$ $IC = I \angle 90^\circ$ $Z = R - jXC$ $Z = 0 - jWL$	
* Node : Meeting point of 2 or more branches.				Distributed Elements: Not, physically separable elements . Ex: Tr. line has distributed R, L, C .		
* Loop / Mesh : Any closed path of branches						

OHM'S LAW, KIRCHHOFF'S LAW, SOURCE TRANSFORMATION

(2)

I OHM'S LAW:

→ States relation b/w V, I, R

$$V \propto I \Rightarrow V = IR$$

Where,

$$R = \frac{\rho l}{A}$$

ρ = Resistivity

l = length

A = Area of x-section

Power Dissipation in Resistor:

$$P = VI = I^2 R = \frac{V^2}{R}$$

$$\text{and } R = \frac{V}{I} = \frac{V^2}{P} = \frac{P}{I^2}$$

$$I = \frac{V}{R} = \frac{P}{IR} = \sqrt{\frac{P}{R}}$$

$$V = IR = P/I = \sqrt{PR}$$

Limitations:

* Can't be applied to non-linear devices

* Non-metallic conductors etc.

II KIRCHHOFF'S LAWS:

→ Solving circuits which cannot be solved by ohm's law.

→ Kirchoff's current law

→ Kirchoff's voltage law


① Kirchoff's current law (KCL)

→ also called point law.

→ Algebraic sum of currents is zero.

→ Incoming current = Outgoing currents.

Illustration:

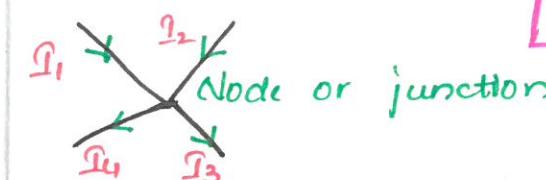

$$\sum I = 0$$

$$I_1 + I_2 - I_3 - I_4 = 0$$

$$(or) I_1 + I_2 = I_3 + I_4$$


(b) Kirchoff's voltage law (KVL)

→ In any closed path/loop/mesh.

→ Algebraic sum of Voltages are equal to zero.

→ Potential rise = Potential drop.

Illustration

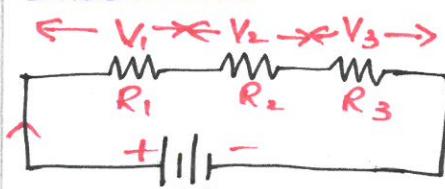


$$\sum V = 0$$

$$V = V - V_1 - V_2 - V_3 = 0$$

$$(or) V = V_1 + V_2 + V_3$$

Sign convention for Voltage:

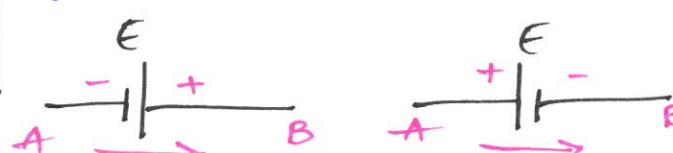


Rise in Voltage Fall in Voltage

(+ε)


(-ε)

III ELECTRICAL Energy Sources

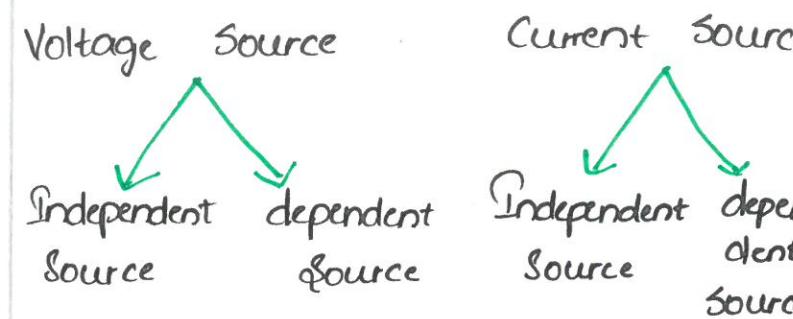


Source Transformation:

Voltage into current source

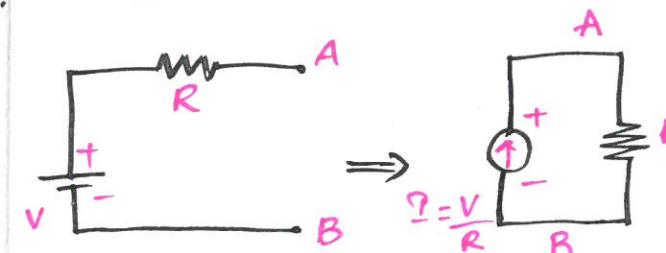

Current into voltage source:

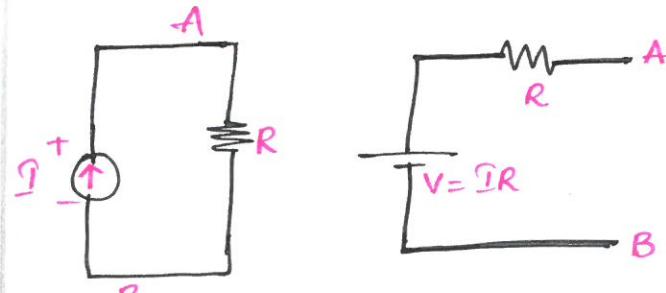

Voltage source in Series


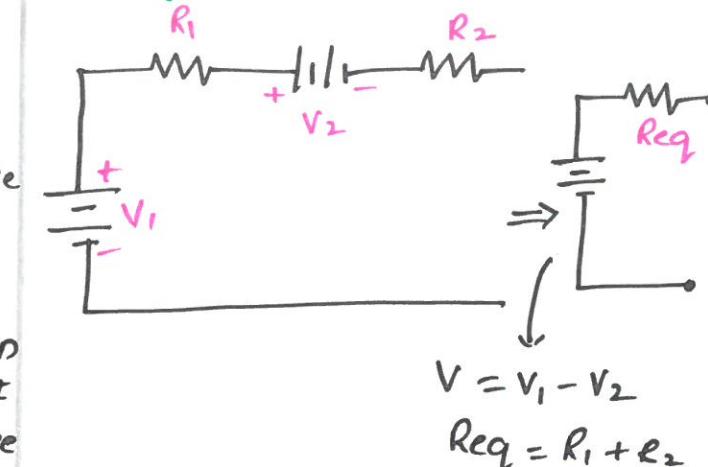
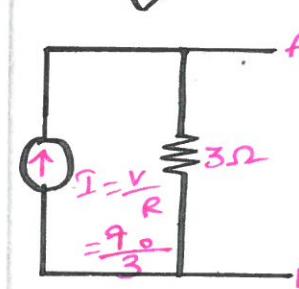
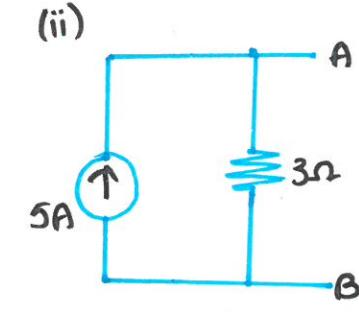




Illustration:

① Convert into equivalent source.

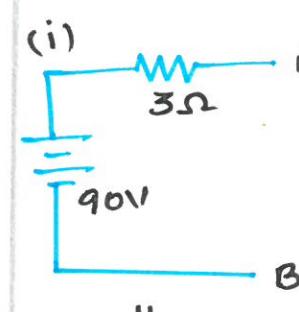


$$= 30A$$

② Obtain single source b/w A & B.

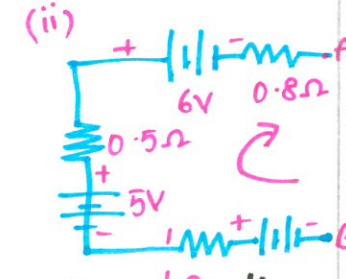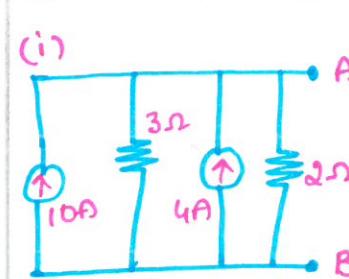


Current Sources in parallel:

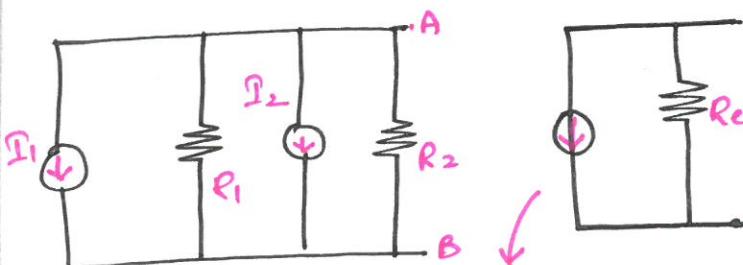

$$I = I_1 + I_2$$

$$Req = \frac{R_1 R_2}{R_1 + R_2}$$

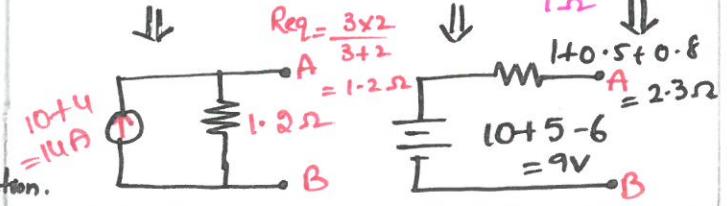* If I_1 & I_2 are in opposite direction.




SERIES AND PARALLEL CIRCUITS

(3)

I NETWORK REDUCTION:

→ Combination of Resistors

(i) Resistance in Series:

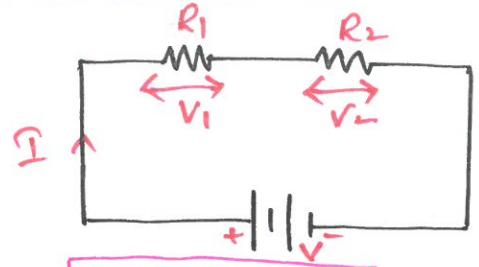

$$R_{eq} = R_1 + R_2 \quad \text{--- (1)}$$

Voltage Division Rule:

→ In series circuit,

I : Same

V = Different.

→ acts as voltage divider.

$$I = \frac{V}{R_1 + R_2} = \frac{V}{R_{eq}}$$

$$V_1 = IR_1 = \frac{V \cdot R_1}{R_1 + R_2} \rightarrow (2)$$

$$V_2 = IR_2 = \frac{V \cdot R_2}{R_1 + R_2} \rightarrow (3)$$

In general,


V.D across interested branch $\left\{ \begin{array}{l} = \frac{\text{Branch resistance}}{\text{Total resistance}} \times \text{applied voltage} \\ = \frac{\text{Branch resistance}}{\text{Total resistance}} \times \text{Voltage} \end{array} \right.$

* If $R_1 = R_2 = R$ (say)

$$R_{eq} = nR \rightarrow (4)$$

Where, n: no. of resistors in series

(ii) Resistance in parallel:

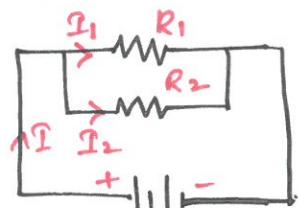

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{eq}} = \frac{R_1 + R_2}{R_1 R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2} \quad \text{--- (5)}$$

Current Division Rule:

→ In parallel circuit,

V ! Same

I : different

→ acts as current divider

$$I = I_1 + I_2 \rightarrow (6)$$

$$I_1 R_1 = I_2 R_2$$

$$I_2 = \frac{I_1 R_1}{R_2} \rightarrow (7)$$

Sub (7) in (6),

$$I = I_1 + I_2 - \frac{R_1}{R_2}$$

$$= I \left(1 + \frac{R_1}{R_2} \right)$$

$\therefore I = \frac{I R_2}{R_1 + R_2}$ and $I_2 = \frac{I R_1}{R_1 + R_2}$ $\rightarrow (8)$

In general, opp. branch current thro' interested branch $\left\{ \begin{array}{l} = \frac{\text{resistance}}{\text{Total resistance}} \times \text{Total current} \\ = \frac{\text{resistance}}{\text{Total resistance}} \times \text{Total current} \end{array} \right.$

* If $R_1 = R_2 = R$ (say)


$$R_{eq} = \frac{R}{n} \rightarrow (9)$$

(iii) Series-parallel circuit:




$$R_{eq} = R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

II. Inductance in Series:

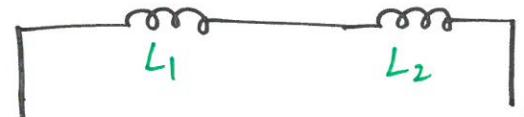

$$L_{eq} = L_1 + L_2$$

Inductance in parallel

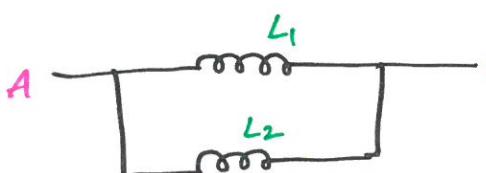


$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2}$$

III. Capacitance in Series:



$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$


Capacitance in parallel:

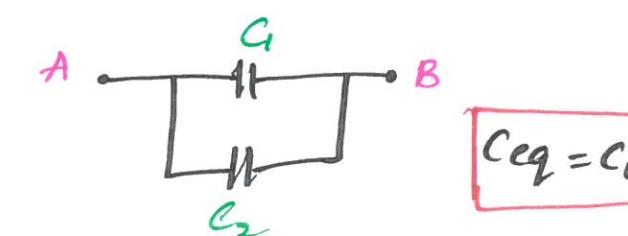

$$C_{eq} = C_1 + C_2$$

Illustrations:

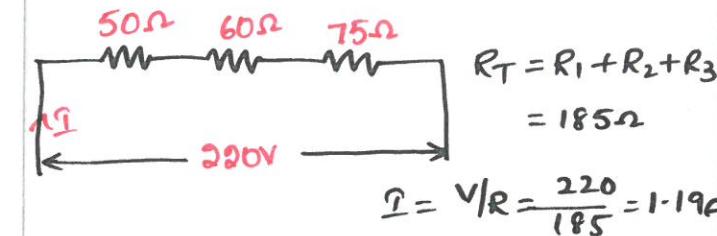① 3 resistors $50\Omega, 60\Omega, 75\Omega$ are connected in series across 220V mains. calculate total resistance current flowing through circuits



② 3 resistors of $6\Omega, 9\Omega, 15\Omega$ are connected in parallel to a 18V supply. calculate current in each branch, supply current, total resistance of network.

$$(a) I_{6\Omega} = \frac{18}{6} = 3A$$


$$I_{9\Omega} = \frac{18}{9} = 2A$$

$$I_{15\Omega} = \frac{18}{15} = 1.2A$$

$$b) I = I_{6\Omega} + I_{9\Omega} + I_{15\Omega} = 6.2A.$$

$$c) R = V/I = 18/6.2 = 2.9\Omega.$$

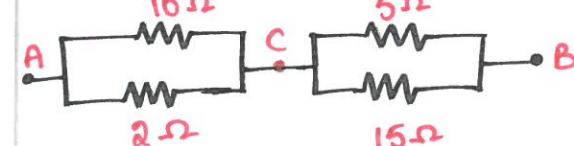③ Determine equivalent resistance between A & B



$$\begin{aligned} \text{Top branch: } & \frac{10 \times 2}{10+2} = 1.67\Omega \\ \text{Bottom branch: } & \frac{5 \times 15}{5+15} = 3.75\Omega \\ \text{Total: } & 1.67 + 3.75 = 5.42\Omega \end{aligned}$$

MESH AND NODAL ANALYSIS - DC CIRCUITS

Problems on Kirchoff's law:

I. Mesh or Loop Analysis:

DC circuits
(only R) AC circuits
(R, L, C)

II Nodal Analysis

DC circuits
(only R) AC circuits
(R, L, C)

I Steps for mesh current analysis:

$$\downarrow \\ \text{O/P} = \mathbf{I} \\ \therefore \mathbf{I}/\mathbf{P} = \mathbf{V}$$

(i) Convert all current sources into its equivalent voltage source.

(ii) Identify no. of independent loop.

(iii) Assume current for each loop.

(iv) Write KVL equation in each loop.

(v) Represent in matrix form.

(vi) Solve the loop for mesh current.

II Steps for Nodal Voltage Analysis:

$$\downarrow \\ \text{O/P} : \mathbf{V} \\ \mathbf{I}/\mathbf{P} : \mathbf{I}$$

(i) Convert voltage source into its equivalent current source.

(ii) Identify No. of nodes.

(iii) Assume voltage for each node.


(iv) Write KCL eq. on each node.

(v) Represent matrix form.

(vi) Solve for node voltages

Illustration: (Mesh Analysis)

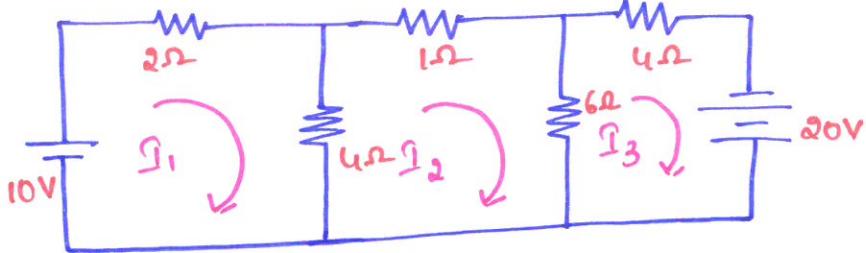① Calculate current thro 6Ω resistor by KVL.



KVL at loop 1 :

$$10 = 2I_1 + 4(I_1 - I_2) = 6I_1 - 4I_2 \rightarrow ①$$

KVL at loop 2

$$0 = I_2(1) + 4(I_2 - I_1) + 6(I_2 - I_3) \rightarrow ②$$

$$0 = 11I_2 - 4I_1 - 6I_3 \rightarrow ②$$

KVL at loop 3

$$20 = 6(I_3 - I_2) + 4I_3$$

$$20 = 10I_3 - 6I_2 \rightarrow ③$$

$$[R] \begin{bmatrix} I \end{bmatrix}_{3 \times 3} = [V]_{3 \times 1}$$

$$\begin{bmatrix} 6 & -4 & 0 \\ -4 & 11 & -6 \\ 0 & -6 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 20 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 6 & -4 & 0 \\ -4 & 11 & -6 \\ 0 & -6 & 10 \end{vmatrix} = 6(110 - 36) + 4(-40 - 0) = 284$$

$$\Delta_1 = \begin{vmatrix} 10 & -4 & 0 \\ 0 & 11 & -6 \\ 20 & -6 & 10 \end{vmatrix} = 10(110 - 36) + 4(0 + 120) = 1220$$

$$\Delta_2 = \begin{vmatrix} 6 & 10 & 0 \\ -4 & 0 & -6 \\ 0 & 20 & 10 \end{vmatrix} = 6(0 + 120) - 10(-40) = 1120$$

$$\Delta_3 = \begin{vmatrix} 6 & -4 & 10 \\ -4 & 11 & 0 \\ 0 & -6 & 20 \end{vmatrix} = 6(220 - 0) + 4(-80) + 10(24 - 0) = 1240$$


$$I_1 = \frac{\Delta_1}{\Delta} = 4.295A$$

$$I_2 = \frac{\Delta_2}{\Delta} = 3.94A$$

$$I_3 = \frac{\Delta_3}{\Delta} = 4.366A$$

② Nodal Analysis:

Apply KCL, find V_1 & V_2 the fig below:

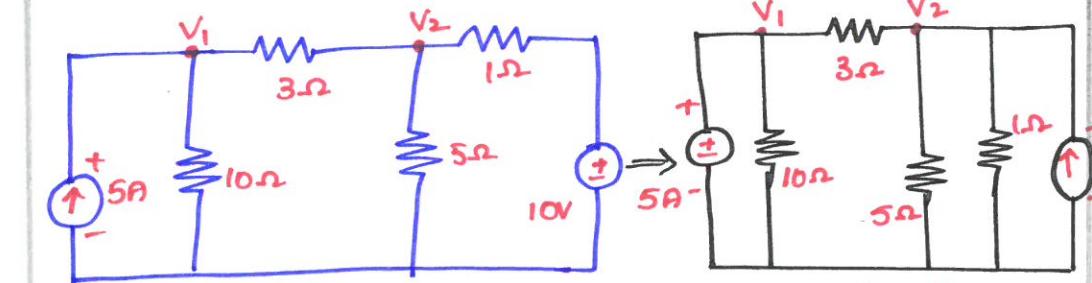

$$I = V/R = 10/1 \\ I = 10A$$

KCL at node 1:

$$5 = \frac{V_1}{10} + \frac{V_1 - V_2}{3}$$

$$3V_1 + 10V_1 - 10V_2 = 150 \rightarrow 13V_1 - 10V_2 = 150 \rightarrow ①$$

KCL at node 2:

$$0 = \frac{V_2 - V_1}{3} + \frac{V_2}{5} + \frac{V_2 - 10}{1}$$

$$0 = 3V_2 + 5V_2 - 5V_1 + 15V_2 - 150 \rightarrow ②$$

$$23V_2 - 5V_1 = 150 \rightarrow$$

By solving ① & ② $\Rightarrow V_1 = 19.86V, V_2 = 10.83V$
(or)

$$[\frac{1}{R}] [V] = [I]$$

$$\left[\left(\frac{1}{10} + \frac{1}{3} \right) \frac{1}{3} \quad \frac{1}{3} \right] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 10 \end{bmatrix}$$

$I_1 = \frac{\Delta_1}{\Delta}$

$$I_2 = \frac{\Delta_2}{\Delta}$$

MESH AND NODAL ANALYSIS - AC CIRCUITS

MESH & NODAL ANALYSIS FOR AC CIRCUITS:-

complex numbers can be represented in

Polar form

* (mag Angle)

* For 'x' & '

Rectangular form

* (Real + jImaginary)

* For '+' & '-'

(i) Rectangular to polar form:

$$\text{Rect. form : } z = (10+j15)$$

$$|z| = \sqrt{10^2 + 15^2} = 18.03$$

$$\angle z = \tan^{-1} \left(\frac{15}{10} \right) = 56.31^\circ$$

$$\Rightarrow \text{polar form : } 18.03 \angle 56.31^\circ$$

(ii) polar to Rectangular form:

$$\text{polar form : } z = 10 \angle 60^\circ$$

$$\text{Real part} = 10 \cos 60^\circ = 5$$

$$\text{Imag. part} = 10 \sin 60^\circ = 8.66$$

$$\Rightarrow \text{Rectangular form: } 5+j8.66$$

Illustration

$$\textcircled{1} \quad z_1 = 10+j10 \Omega \quad \& \quad z_2 = 20-j30 \Omega$$

$$z_1+z_2 = (10+20)+j(10-30) \\ = (30-j20) \Omega$$

$$z_1-z_2 = (-10+j40) \Omega$$


$$\textcircled{2} \quad z_1 = 10 \angle 60^\circ \Omega, \quad z_2 = 20 \angle 30^\circ \Omega$$

$$z_1 = z_2 = 10 \times 20 \angle 60^\circ + 30^\circ = 200 \angle 90^\circ$$

$$z_1/z_2 = \frac{10}{20} \angle 60^\circ - 30^\circ = 0.5 \angle 30^\circ$$

Determine the real power output of the source shown in fig. below by Nodal analysis and verify the result by using Mesh analysis.

(i) By Nodal Analysis:

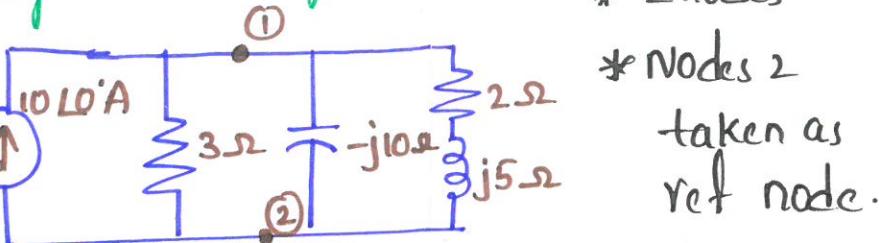

- * 2 nodes
- * Nodes 2 taken as ref node.

$$\text{KCL at node 1, } \frac{V_1}{3} + \frac{V_1}{-j10} + \frac{V_1}{2+j5} = 10 L0^\circ$$

$$\left(\frac{1}{3} + \frac{j}{10} + \frac{1}{2+j5} \right) V_1 = 10 L0^\circ$$

$$\left[\frac{1}{3} + \frac{j}{10} + \frac{2-j5}{2^2 - (j5)^2} \right] V_1 = 10 L0^\circ$$

$$\left[\frac{1}{3} + \frac{j}{10} + \frac{2-j5}{29} \right] V_1 = 10 L0^\circ$$


$$(0.402 - j0.072) V_1 = 10 L0^\circ$$

$$(0.41 \angle -10.2^\circ) V_1 = 10 L0^\circ$$

$$V_1 = \frac{10 L0^\circ}{0.41 \angle -10.2^\circ} = 24.4 \angle 10.2^\circ V$$

$$\therefore \text{Real output of source} = V_1 I \cos(10.2^\circ) \\ = 24.4 \times 10 \times \cos 10.2^\circ = 240 W$$

(ii) By Mesh current Analysis:

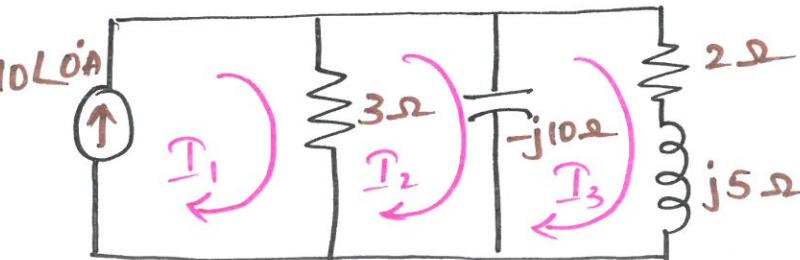

Here $I_1 = 10 L0^\circ$ in loop 1 — (1)

KVL at loop 2,

$$+ (I_2 - I_3)(-j10) + (I_2 - I_1)3 = 0$$

$$-j10 I_2 + j10 I_3 + 3 I_2 - 3 I_1 = 0$$

$$(3-j10) I_2 + j10 I_3 = 3 I_1 = 3(10) = 30 \quad \text{--- (2)}$$

KVL at loop 3,

$$(2+j5) I_3 + (I_3 - I_2)(-j10) = 0$$

$$2 I_3 + j5 I_3 - j10 I_3 + j10 I_2 = 0$$

$$j10 I_2 + (2-j5) I_3 = 0$$

Substitute (3) in (2)

$$(3-j10) I_2 + j10 \left(\frac{-j10 I_2}{(2-j5)} \right) = 30$$

$$\left[3 - j10 + \frac{100}{(2-j5)} \right] I_2 = 30$$

$$(3-j10 + 6.9 + j17.24) I_2 = 30$$

$$12.27 \angle 36^\circ I_2 = 30 \Rightarrow I_2 = \frac{30}{12.27 \angle 36^\circ}$$

$$\Rightarrow I_2 = 2.45 \angle -36^\circ A$$

$$\therefore I_3 \Omega = I_1 - I_2 = 10 - 2.45 \angle -36^\circ = 10 - (1.98 - j1.46) \\ = 8.02 + j1.46 = 8.15 \angle 10.3^\circ A$$

$$V_3 \Omega = I_3 \Omega \times R = 8.15 \angle 10.3^\circ \times 3 \\ = 24.45 \angle 10.3^\circ V$$

$$\text{Power from the source} = 24.45 \times 10 \cos 10.3^\circ \\ = 240.6 \text{ watts} \quad \text{--- (B)}$$


(A) = (B), Hence verified.

TRANSFORMATION, AC FUNDAMENTALS

(6)

Star - Delta Transformation (Y) (Δ)

* Also called T and π transformation.

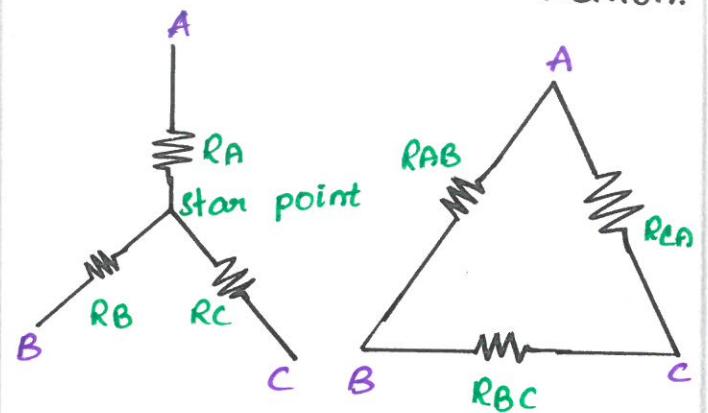

I Δ to Y transformation

Given: R_{AB} , R_{BC} , R_{CA}

To find: R_A , R_B , R_C

$$R_A = \frac{R_{AB} R_{CA}}{\Sigma R_{AB}}$$

$$R_B = \frac{R_{AB} R_{BC}}{\Sigma R_{AB}}$$

$$R_C = \frac{R_{BC} R_{CA}}{\Sigma R_{AB}}$$

II Y to Δ transformation:

Given: R_A , R_B , R_C


To find: R_{AB} , R_{BC} , R_{CA}

$$R_{AB} = R_A + R_B + \frac{R_A R_B}{R_C}$$

$$R_{BC} = R_B + R_C + \frac{R_B R_C}{R_A}$$


$$R_{CA} = R_C + R_A + \frac{R_C R_A}{R_B}$$

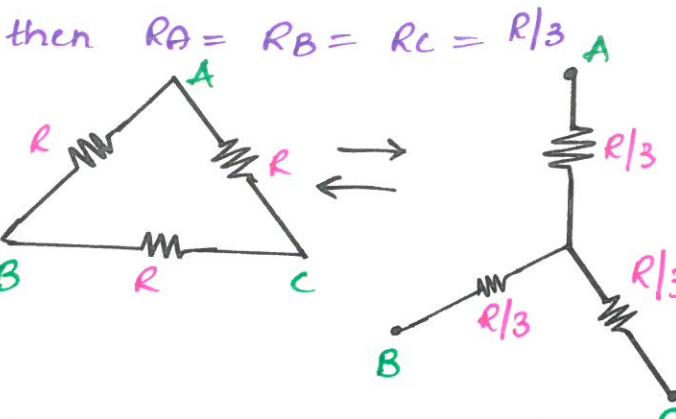(i) If $R_{AB} = R_{BC} = R_{CA} = R$ (say)




(ii) If $R_A = R_B = R_C = R$ (say)

then $R_{AB} = R_{BC} = R_{CA} = 3R$






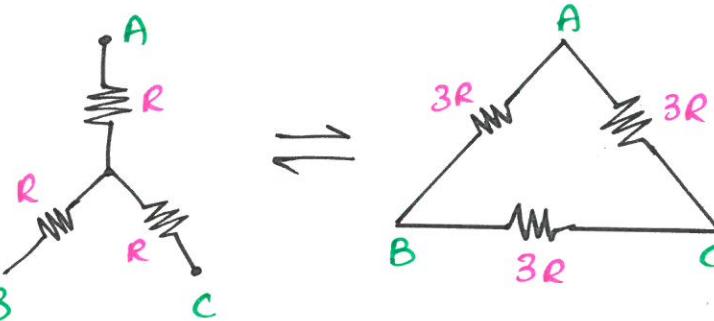


Illustrations:



Convert Δ to Y

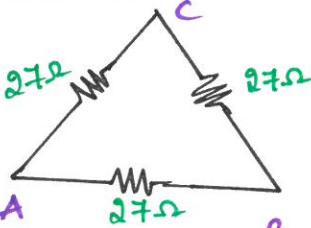


Convert Y to Δ

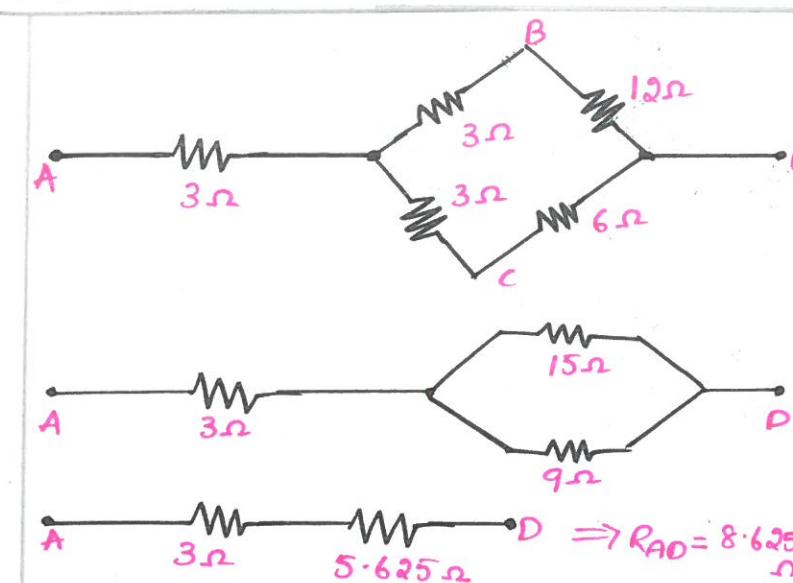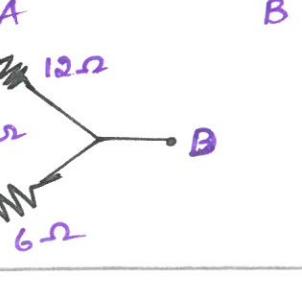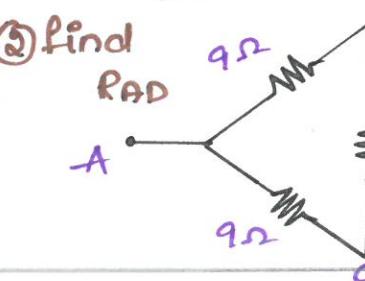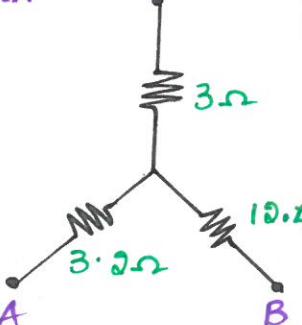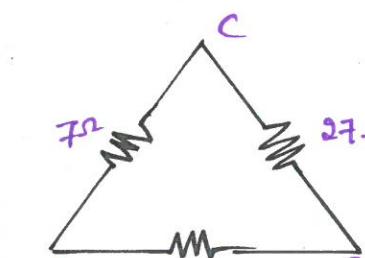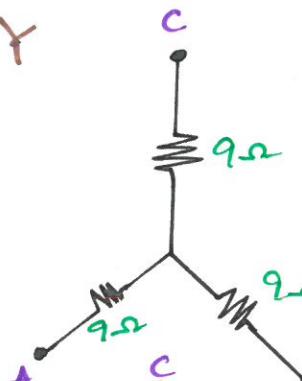

③ find R_{BC}

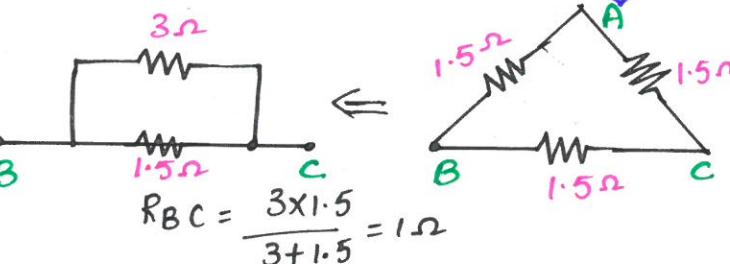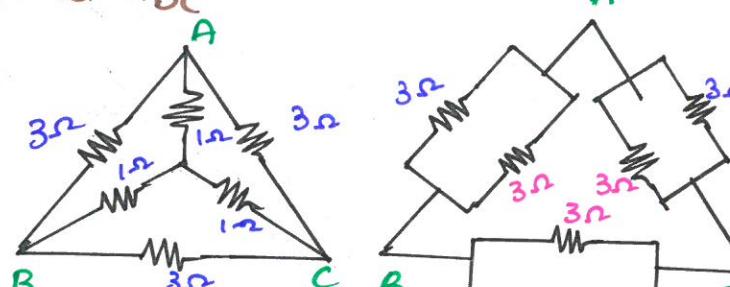

④ find R_{AB}

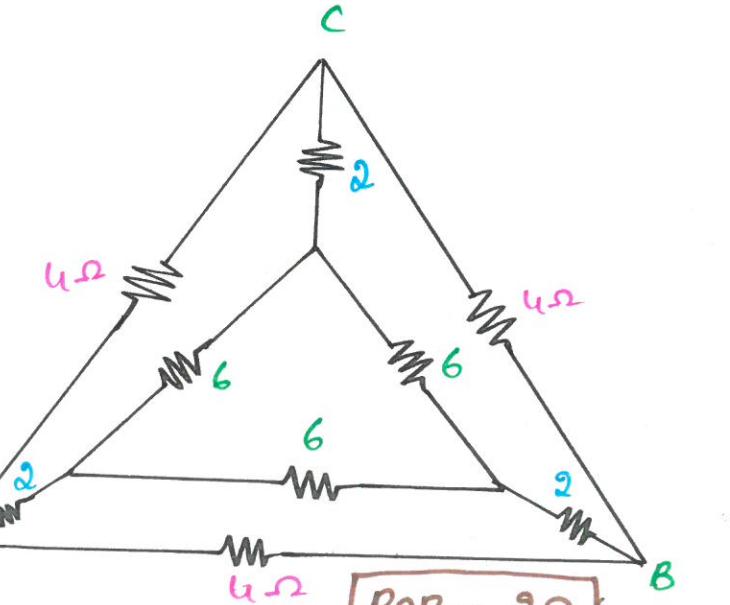

fundamentals of AC Circuits:

* AC quantity has magnitude & angle.

* Varying w.r.t. to time.

* Represented in 3 ways

- Effective value (RMS)

- Average value.

- Peak value.

* Amplitude : max. value of an ac quantity.

* Cycle : Set of +ve and -ve halves.


* Frequency : No. of cycles/sec. Hertz or c/s.

* Period : Time taken to complete one cycle $T = \frac{1}{f}$.

* Peak Value : Max. possible value.

* phase : Time that has elapsed from zero point of reference.

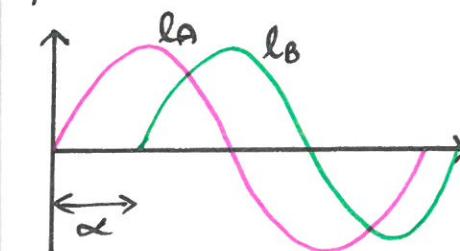* phase difference : To compare phases of 2 waveforms.



lA : Starts & progress ahead leading

lB : Starts & progress behind lagging.

DEFINITION, ANALYSIS OF STEADY-STATE AC CIRCUITS

(7)

I. RMS Value:

* Root Mean Square Value

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V^2 dt}$$

$$I_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} I^2 dt}$$

$\boxed{\text{Area Under Squared Wave}}$

For Sinewave, $V_{rms} = \frac{V_m}{\sqrt{2}}$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

II. Average Value:

Average = Area Under One Complete Cycle / Period

$$V_{ave} = \frac{1}{T} \int_0^T V dt \text{ or } \frac{1}{2\pi} \int_0^{2\pi} V dt$$

For instantaneous values,

$$I_{ave} = \frac{i_1 + i_2 + \dots + i_n}{n}$$

For Sinewave, $V_{ave} = \frac{2V_m}{\pi}$

$$I_{ave} = \frac{2I_m}{\pi}$$

III. Form Factor (K_f):

$$K_f = \frac{\text{RMS Value}}{\text{Ave. Value}} = 1.11 \text{ for Sinewave}$$

IV. Peak Value or factor (K_p):

$$K_p = \frac{\text{Peak Value}}{\text{RMS Value}} = 1.414 \text{ for Sinewave}$$

STEADY STATE ANALYSIS OF AC CIRCUITS

* AC Quantity: Magnitude & Phase

* Complex Operator: $j = \sqrt{-1}$

Properties of j :

$$\begin{aligned} j &= 90^\circ, \text{ CCW} = \sqrt{-1} \\ j^2 &= 180^\circ, \text{ CCW} = -1 \\ j^3 &= 270^\circ, \text{ CCW} = -j \\ j^4 &= 360^\circ, \text{ CCW} = 1 \end{aligned}$$

Impedance (Z):

$$\begin{aligned} Z &= R + j(X_L - X_C) \text{ ohms.} \\ |Z| &= \sqrt{R^2 + (X_L - X_C)^2} \\ \phi &= \tan^{-1} \left(\frac{X_L - X_C}{R} \right) \end{aligned}$$

Imp. triangle

Admittance (Y): $Y = \frac{1}{Z} = \frac{1}{R + j(X_L - X_C)}$ (mho)

Instantaneous Power:

$$P(t) = V(t) \cdot i(t)$$

Average Power (P):

* Called Real or Active Power

* Unit is watt or kW

$$P = V I \cos \phi = V_{rms} I_{rms} \cos \phi$$

Reactive Power (Q):

* Called useless power


* Unit is VAR or kVAR

$$Q = V I \sin \phi = V_{rms} I_{rms} \sin \phi$$


Apparent Power (S):

* Unit is VA or kVA

$$S = V I = V_{rms} I_{rms}$$

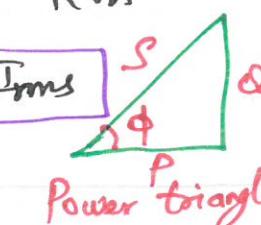

I. Analysis of 'R' circuit:

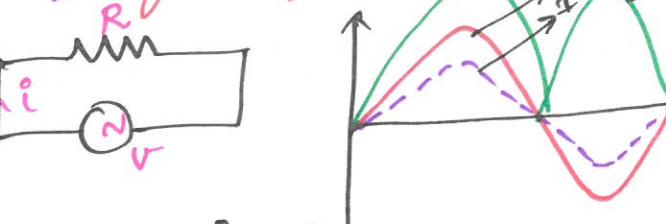

$$V = V_m \sin \omega t$$


$$i = I_m \sin \omega t ; I_m = \frac{V}{R}$$

$$\phi = 0 ; \cos \phi = \text{pf} = \frac{R}{Z} = 1$$

$$Z = R$$

$$P_{ave} = \frac{V_m I_m}{2}$$

II. Analysis of 'L' circuit

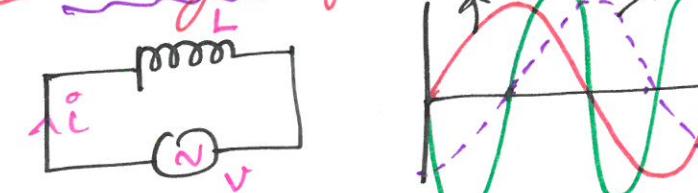

$$V = V_m \sin \omega t$$

$$i = I_m \sin(\omega t - 90^\circ) ; I_m = \frac{V}{X_L}$$

$$\phi = 90^\circ, 'i' \text{ lags } 'v' \text{ by } 90^\circ$$

$$\cos \phi = 0$$

$$Z = j\omega L = jX_L$$

$$P_{ave} = 0$$

$\boxed{I(\text{lag})}$

III. Analysis of 'C' circuit



$$V = V_m \sin \omega t$$

$$i = I_m \sin(\omega t + 90^\circ)$$

$$'i' \text{ leads } 'v' \text{ by } 90^\circ, \phi = 90^\circ, \cos \phi = 0$$

$$Z = -jX_C$$

$$P_{ave} = 0$$

$\boxed{I(\text{lead})}$

IV. Analysis of RL Series Circuit



$$\begin{aligned} \bar{V} &= \bar{V}_R + \bar{V}_L \\ &= I(R + X_L) \end{aligned}$$

$$\begin{aligned} Z &= R + jX_L = \sqrt{R^2 + X_L^2} \cdot \tan^{-1} \left(\frac{X_L}{R} \right) \\ &= |Z| \angle \phi \end{aligned}$$

$$|V| = \sqrt{V_R^2 + V_L^2}$$

$$\begin{aligned} I &= \frac{V}{Z} \\ \phi &= \tan^{-1} \frac{\omega L}{R} \Rightarrow \cos \phi = \frac{R}{Z} \end{aligned}$$

IV. Analysis of RC Series Circuit



$$\begin{aligned} V_R &= IR \\ V_C &= IX_C \end{aligned}$$

$$\bar{V} = \bar{V}_R + \bar{V}_C = I(R - jX_C)$$


$$Z = R - jX_C = \sqrt{R^2 + X_C^2}$$

$$\phi = \tan^{-1} \left(\frac{X_C}{R} \right)$$

$$P_f = \cos \phi = \frac{(R)}{|Z|}$$

$$I = \frac{V}{Z}$$

VI. Analysis of RLC Series Circuit

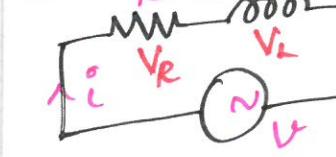

$$\begin{aligned} V_R &= IR \\ V_L &= IX_L \\ V_C &= IX_C \end{aligned}$$

$$\bar{V} = \bar{V}_R + \bar{V}_L + \bar{V}_C = I(R + j(X_L - X_C))$$

$$Z = R + j(X_L - X_C) = \sqrt{R^2 + (X_L - X_C)^2} \cdot \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

$$I = \frac{V}{Z} ; P_f = \cos \phi = \frac{R}{|Z|}$$

$$X_L < X_C \text{ Inductive} ; X_L > X_C \text{ Capacitive}$$

ELECTRICAL MACHINES - DC Generators: LAWS, CONSTRUCTION, OPERATION

8

Lenz's Law:

$$E = -N \frac{d\phi}{dt}$$


where, E : Induced emf

N : No. of turns in coil

$d\phi$: change in flux

dt : change in time


Fleming's Right Hand Rule (FRH)

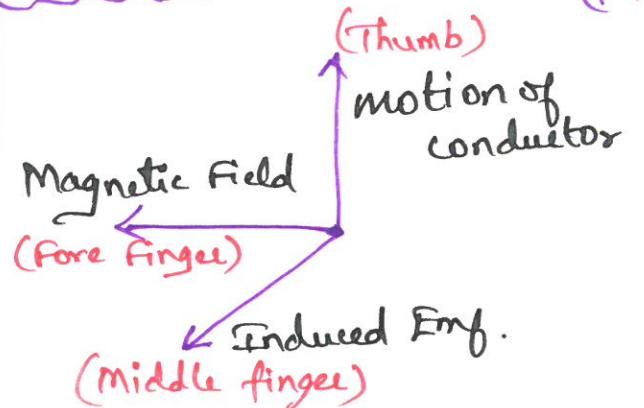

* Used to determine the direction of induced emf.

* Employed in DC Generators.

Fleming's Left Hand Rule (RLH)

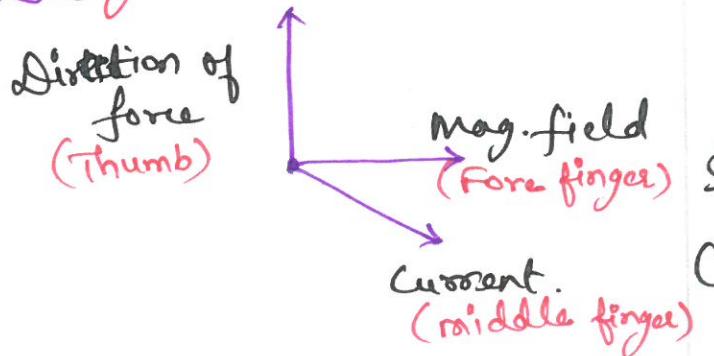

* Employed in DC motors

* To determine direction of force.

Faraday's law:

Whenever a conductor cuts the magnetic flux, dynamically induced emf is produced in the conductor.

Dc Machines

DC Generators


- * Mechanical to Electrical
- * Faraday's Law + FRH rule.

DC Motors


- * Electrical to mechanical
- * Faraday's law + FLH Rule

CONSTRUCTION OF DC MACHINE

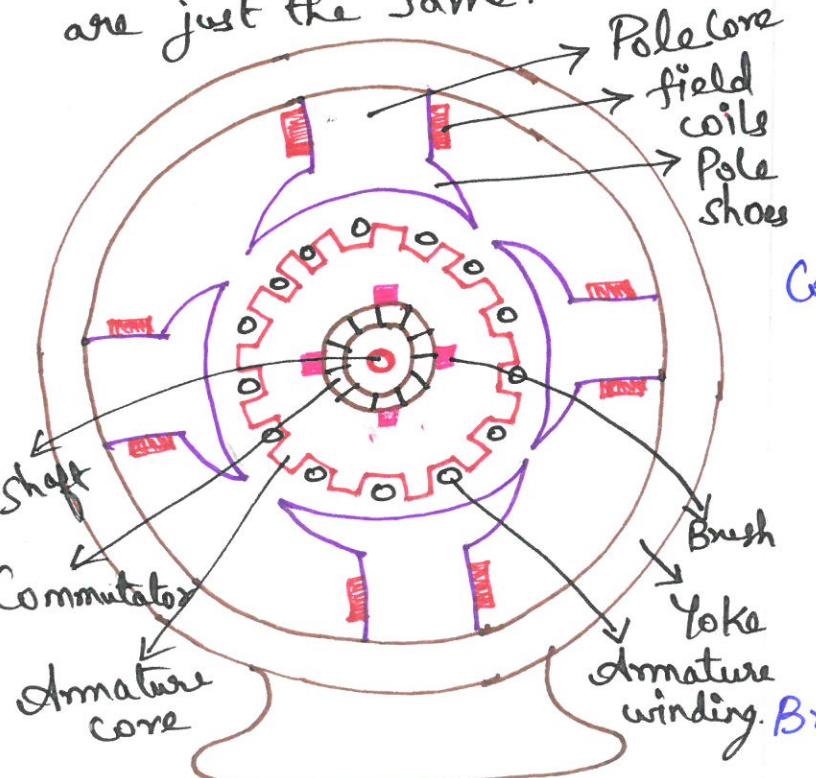- * Construction of motor & generators are just the same.



PRINCIPLE OF OPERATION

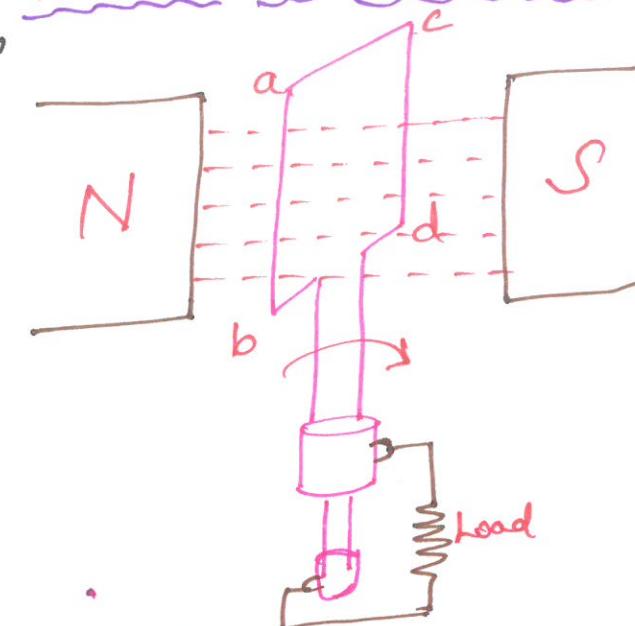

Yoke:

- Provides mech. Support
- Provide path for mag. flux
- Made of thin steel lamination to reduce loss

Pole Core:

- Field windings are mounted on pole core.
- Made of thin steel lamination

Pole shoe:

- Provide uniform distribution of mag. flux
- made of thin steel laminations

Field coils:

- Made of copper wire
- provides the mag. field

Arm. Core:

- Mounted on shaft
- windings are mounted in slots of arm. core
- cylindrical shape

Arm. Coils:

- Provides emf when used as generator.


- Rotates the shaft.
- provides torque when used as motor.
- Made of copper wire

Commutator:

- Converts AC to DC emf.
- collects current from arm. coil
- Provides unidirectional torque (for Motor)
- Provides unidirectional emf. (for Generator)

Brushes:

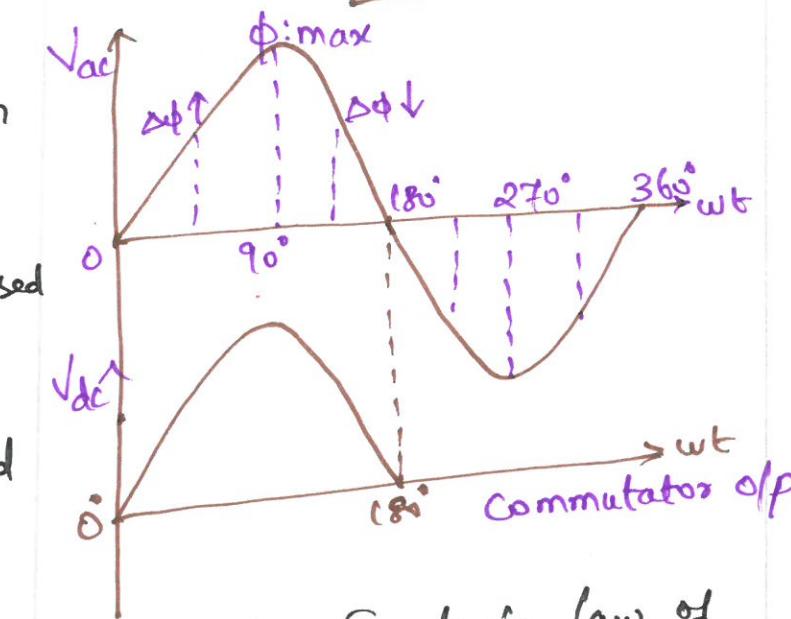- stationary & press on commutator
- carry current towards/away from commutator
- made of carbon or copper.



* Principle: Faraday's law of Electromagnetic Induction.

* Emf. induced in arm. coil is Ac. Commutator converts Ac into Dc.

Types of Armature Winding:

(i) Lap Winding:

$$P = A$$


P : No. of poles
A : No. of parallel paths

(ii) Wave Winding:

$$A = 2$$

PRINCIPLE OF OPERATION OF MOTOR

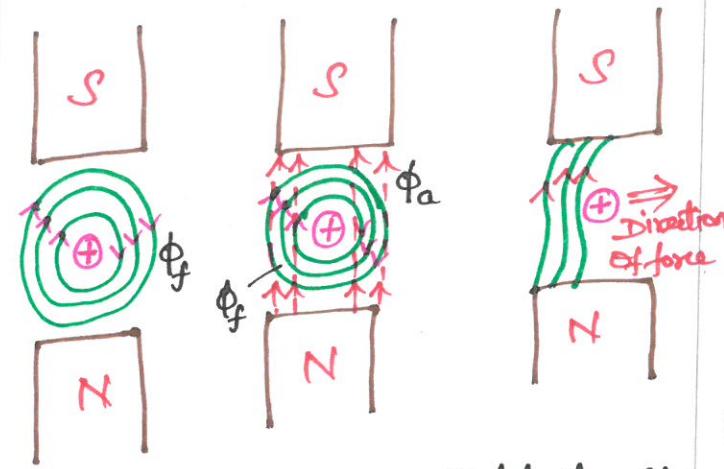- * Converts Elec. Energy into Mechanical Energy.
- * Employs Faraday's law + FLH rule



- * I_{field} produces field flux (ϕ_f)
- * $I_{\text{arm.}}$ produces armature flux (ϕ_a)
- * ϕ_f and ϕ_a interacts with each other.
- * LHS : Both flux aids
- RHS : Both flux opposes
- * LHS flux produces twisting force called Torque.
- * Motor starting Rotating.


Significance of Back Emf (E_b):

- * After every motoring, there is a generator action.
- * Induces emf (E_b)
- * E_b opposes applied voltage

$$E_b = \frac{\phi Z N}{60} \cdot \frac{P}{A}$$

TORQUE EQUATION

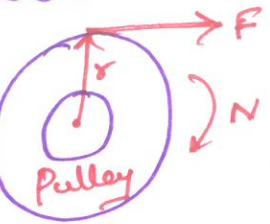Let
 r : Radius
 F : Circumferential force
 N : Speed



$$\therefore \text{Torque} = T = (F \times r) \text{ NM.}$$

Work done by the force / sec,
 $= \text{Force} \times \text{distance}$
 $= F \times 2\pi r$

$$\begin{aligned} \text{Power developed} &= F \times (2\pi r) \times N \\ &= T \times 2\pi N. \end{aligned}$$

$$\text{If 'N' is in rpm, } w = \frac{2\pi N}{60} \text{ rad/sec.}$$

$$\Rightarrow P = \frac{2\pi N T}{60} \quad \text{--- (1)}$$

Let

Armature Torque = T_a

$$\therefore P = E_b \cdot I_a \quad \text{--- (2)}$$

$$(1) = (2), E_b \cdot I_a = \frac{2\pi N T}{60}$$

$$T_a = \frac{1}{2\pi} \cdot \phi I_a \cdot \frac{PZ}{A} \text{ NM.}$$

or


$$T_a = 0.159 \phi I_a \frac{ZP}{A} \text{ NM}$$

Types of DC motor:

- Shunt motor
- Series motor
- Compound motor
 - Long shunt
 - Short shunt

DC MOTORS: PRINCIPLE OF OPERATION, EQUATIONS.

(1) DC Shunt motor:

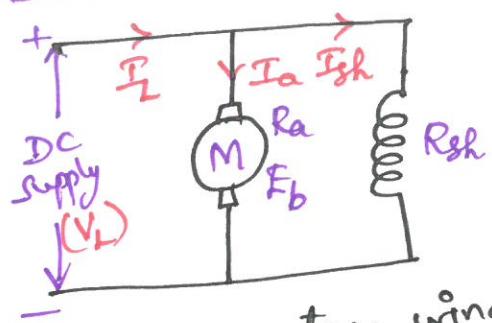

- * field & armature windings are in Parallel
- * Called as Constant speed motor.

$$\text{By KCL, } I_L = I_a + I_{sh}$$

$$\text{By KVL, } V_L = E_b + I_a R_a + BCD$$


$$E_b = \frac{\phi Z N}{60} \cdot \frac{P}{A}$$

$$\text{and } I_{sh} = \frac{V_L}{R_{sh}}.$$

Applications:

Lathes, Centrifugal pumps, fans, Blowers, Reciprocating pumps etc.

(2) DC Series Motor:

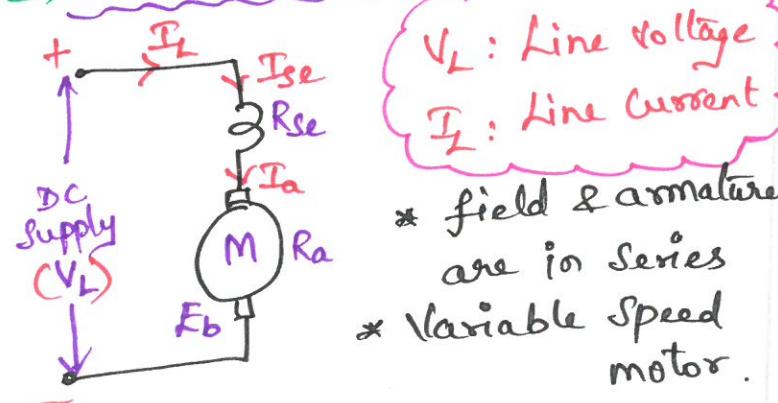

V_L : Line voltage
 I_L : Line current

- * field & armature are in series
- * Variable speed motor.

$$\text{By KCL, } I_L = I_{se} = I_a$$

$$\text{By KVL, } V_L = E_b + I_a (R_a + R_{se})$$


Applications:

Trolley, Cranes, hoists, lifts, Conveyors, Electrical Locomotives etc.

(3) DC Compound motor:

- * Part of field winding is in Series
- * Remaining part is in parallel with armature.

Long shunt Comp. motor:

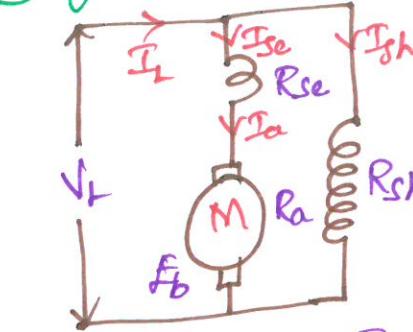

$$\text{By KCL, } I_L = I_{se} + I_{sh}$$

$$I_a = I_{se}$$


$$\text{By KVL, } V_L = E_b + I_a (R_a + R_{se}) + BCD$$

$$\text{and } I_{sh} = \frac{V_L}{R_{sh}}.$$

Applications:

Elevators, Conveyors, Rolling mills etc

short shunt Comp. motor:

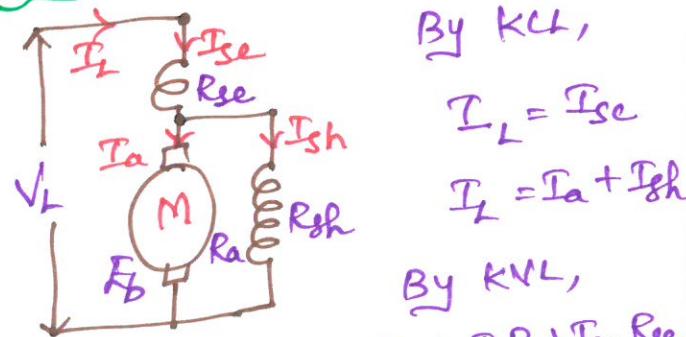

$$\text{By KCL, } I_L = I_{se}$$

$$I_L = I_a + I_{sh}$$

$$\text{By KVL, } V_L = E_b + I_a (R_a + R_{se}) + BCD$$

$$\text{and } I_{sh} = \frac{E_b - I_a R_a}{R_{sh}}.$$

Applications:

R & D and Defence applications.

STARTERS AND ITS TYPES

STARTERS:

- * Start and stop the motor
- * Limit inrush current when necessary
- * Permit automatic control when required
- * Protect motor and other equipments from Over voltage, no voltage, Under voltage etc.

Need of starters:

W.K.T, In motors,

$$V = E_b + I_a R_a$$

- * At the time of start,


$$E_b = 0, \because N=0$$

V : Applied Voltage
 E_b : Back Emf
 I_a : Arm. Current
 R_a : Arm. Resistance
 $R_a \leq 3\Omega$

- * Since ' R_a ' is very low, ' I_a ' becomes large.
- * Huge ' I_a ' may damage the machine.
- * Starters are nothing but Series Connected Resistors.
- * To avoid the damage, a suitable DC motor starter must be used.

Types of DC motor starters:

I. Two point starter:

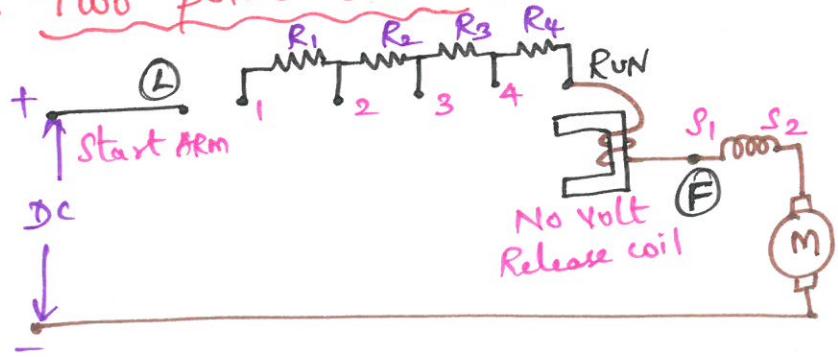


- * Used in DC series motor

- * 2 points are: Line (L) and field (F)

- * Start arm is moved from left to right. (Start) (Run)
- * Resistor connected at starting, then reduced gradually.
- * No Volt Release (NVR) coils hold the start arm to run position, and leaves it when voltage is lost.


II. Three Point starter:

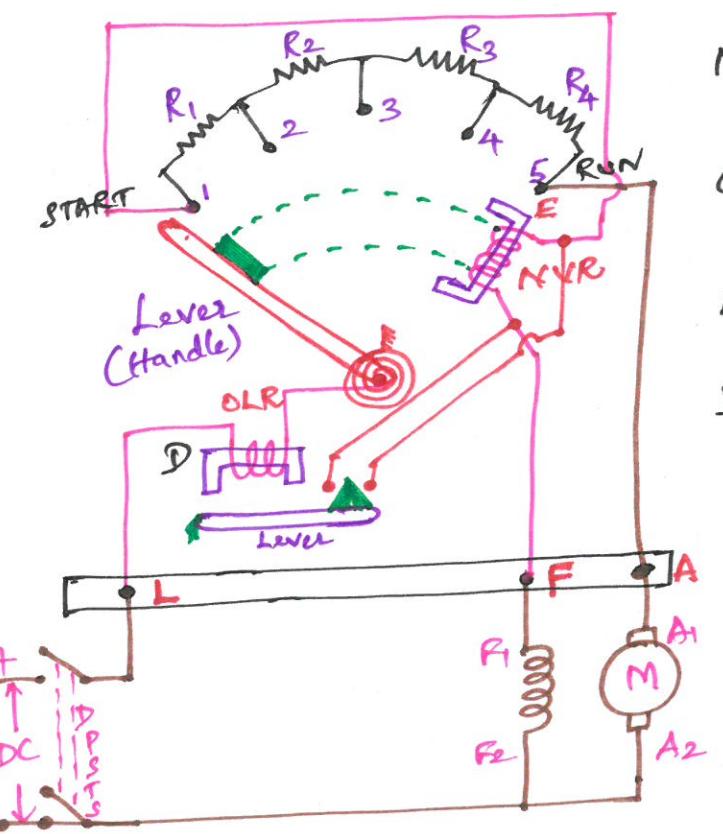

- * DC supply is connected - lever at position ①
- * Field directly connected to supply
- * Armature winding connected via R_1, R_2, R_3, R_4 .
- * During starting: full 'R' connected
- * Lever moved from pos. ① to ② (Run)
- * At pos. ③, all starting 'R' are removed
- * Now, Arm. Connected across supply.
- * NVR: Holds handle or lever at run position. Releases when there is no power.

- * Moving from start to run, I_{sh} decreases hence, NVR releases handle respectively.
- * OLR: 'D' gets activated, when overcurrent flows, which short circuits 'E', releases the handle to start.

III. Four point starter:

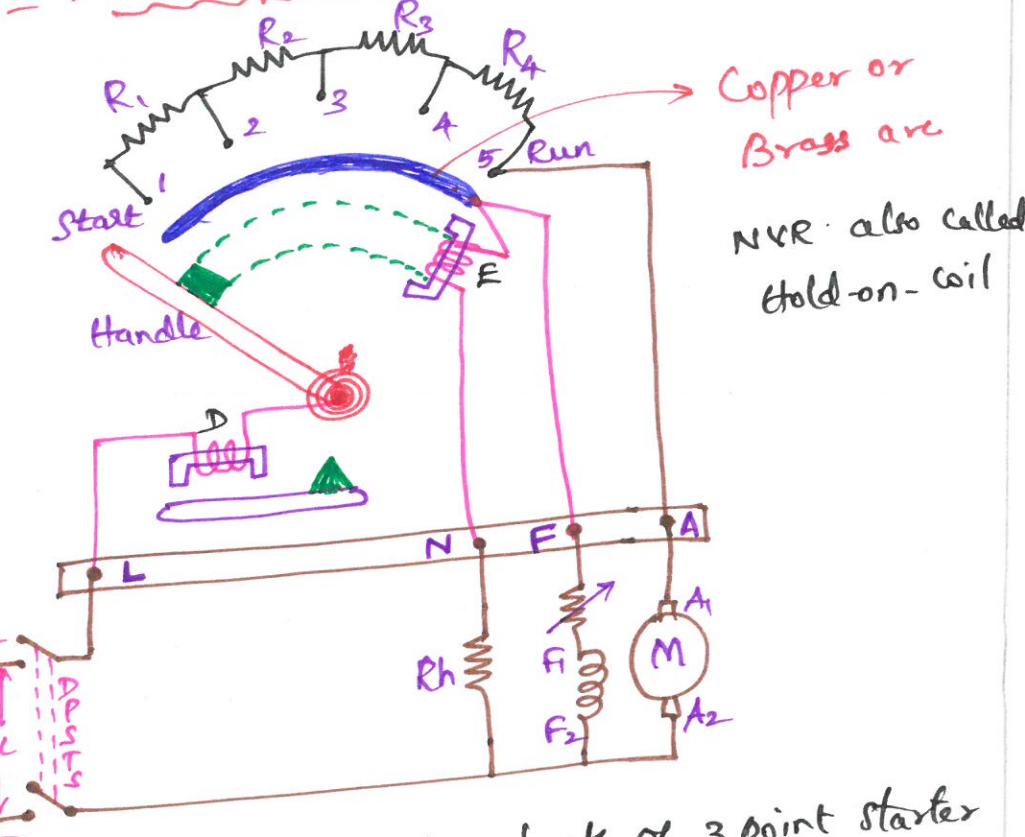

- * Eliminates the drawback of 3 point starter
- * field flux can be varied conveniently to increase the speed.

$$\phi_f \propto \frac{1}{N}$$

- * Field coil is not connected in series with NVR.

- * Field gets direct supply, as lever touches brass arc.
- * NVR connected with current limiting resistor.

PROTECTION CIRCUITS OF STARTERS!

NVR and OLR.

SINGLE PHASE TRANSFORMERS: CONSTRUCTION, OPERATION, EMF EQUATION

(12)

Faraday's law:

$$E = N_s \cdot \frac{d\phi}{dt}$$


where, N_s : No. of turns.

TRANSFORMER:

- * Static Electrical Machines - No Rotating parts
- * Transfers Electrical Energy from one Circuit to another.
- * With Constant frequency.
- * Works on Mutual Induction principle.

CONSTRUCTION:

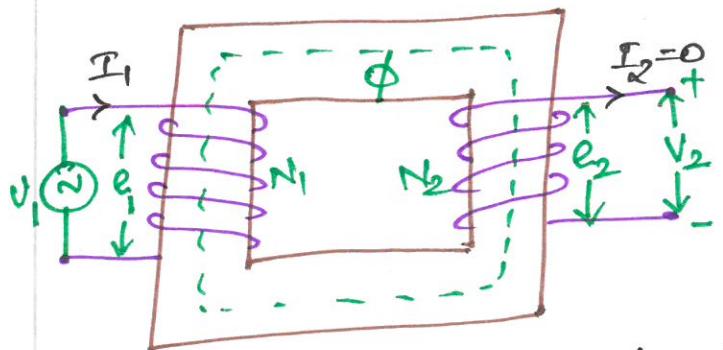- * Consists of 2 windings
- * Insulated from each other
- * Both are wound on a common Core, made of mag. material



- * V_1, V_2 : Primary & Secondary Voltage
- * I_1, I_2 : Primary & Secondary Current
- * N_1, N_2 : Primary & Secondary no. of turns
- * e_1, e_2 : Primary & Secondary induced emf
- * Φ : Magnetic flux


Major Parts:

- (i) Magnetic core
- (ii) Windings or coils

Magnetic Core:

- * Core is either square or rectangular type.
- * Further divided into 2 parts
 - yoke: Horizontal position
 - Limb: Vertical position.

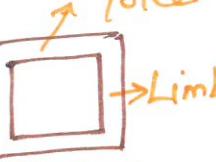* Made of Laminated sheets of silicon steel




Reduces Eddy current loss

* Generally uses high grade silicon steel (0.3 to 0.5 mm thick)

To reduce hysteresis loss

* Laminations are being insulated from each other by a varnish or an oxide layer.

Windings:

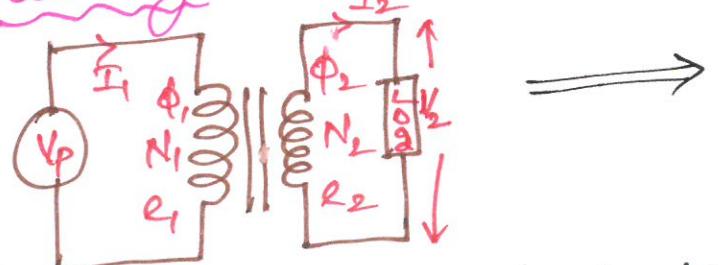

* Primary: winding connected to AC Supply

* Secondary: winding connected to Load

* Made of Cu or Al.

* Coils are wound on Limbs.


* To avoid magnetic leakage,

Part of each winding wound on both limbs.


Other parts: - Insulation of coils

- Conservator tank & Expansion Vent
- Bushings
- Buchholz Relay
- Breathers
- Cooling arrangement

Types of Transformers

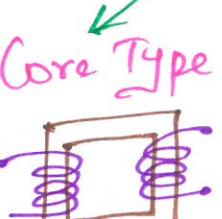

Core Type

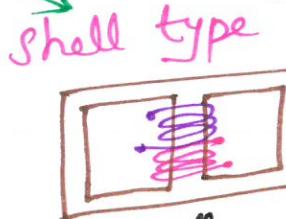

Shell type

- * Core is surrounded by windings
- * Windings are surrounded by core

PRINCIPLE OF OPERATION:

* Principle of mutual inductance

* When V_1 is connected

Forces " I_1 " to flow thru' Primary

Induces ϕ , $\propto I_1$ according to N_1

$$\therefore e_1 = N_1 \frac{d\phi}{dt}$$

ϕ , links Secondary coil via magnetic core.

Induces ϕ_2 according to N_2

$$\therefore e_2 = N_2 \frac{d\phi_2}{dt}$$

$\phi_2 < \phi$, due to leakage flux.


If secondary is closed,
 e_2 forces I_2 to flow.

V_2 can be controlled by ratio of N_1 & N_2 .

Transformation Ratio (K)

$$K = \frac{V_2}{V_1} = \frac{N_2}{N_1} = \frac{E_2}{E_1} = \frac{I_1}{I_2}$$

EMF EQUATION OF TRANSFORMER

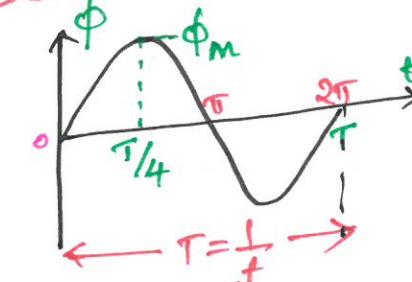

* ϕ_m is max. flux in core in wb.

$$\phi_m = B_m \times A$$

* Consider 1 quarter of cycle,

$$d\phi = \phi_m - 0 = \phi_m$$

$$dt = \frac{T}{4} = \frac{1}{4f}$$

$$\text{Average emf/turn} = \frac{d\phi}{dt} = \frac{\phi_m}{(\frac{1}{4f})} = 4f\phi_m$$

* ϕ varies sinusoidally,

$$\therefore \text{Form factor} = \frac{\text{rms value}}{\text{ave. value}} = 1.11$$

$$\Rightarrow \text{Rms value of emf per turn} = 1.11 \times 4f\phi_m$$

$$E_1 = 4.44 f \phi_m N_1 \text{ Volts}$$

$$E_2 = 4.44 f \phi_m N_2 \text{ Volts}$$

3. SEMICONDUCTOR DEVICES.



Semiconductor devices.

① PN Diode

② ZENER DIODE

①

Theory of PN Junction

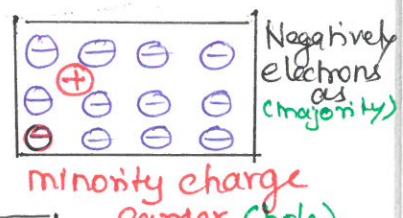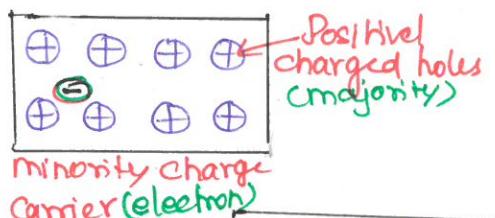


Symbol!




operation of PN Junction.

Forward Bias.

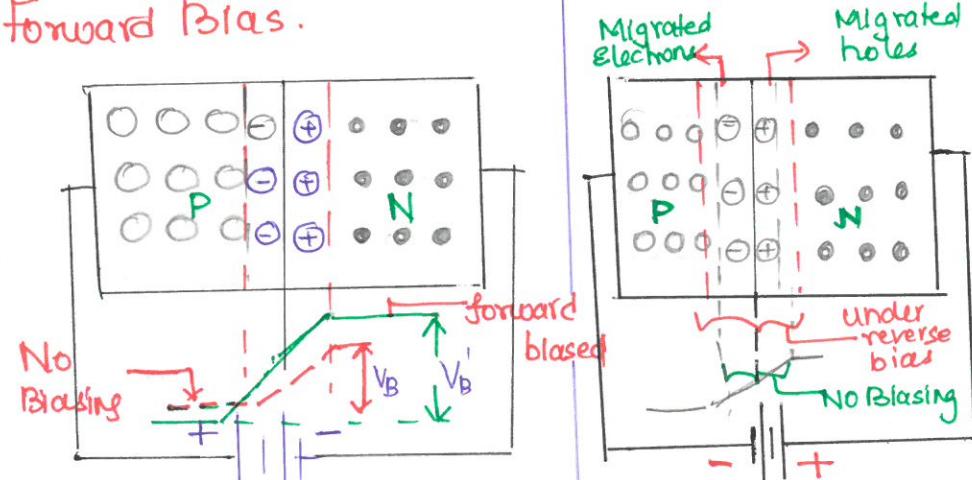

VI characteristics

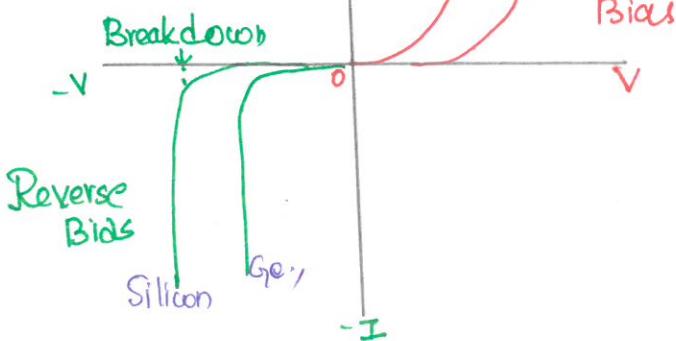



③ Zener diode

① A Diode is Reverse biased, depletion layer widens..

② Setup a Large potential barrier- prevents majority carriers from one side to other. Junction breakdown is of


- (i) Zener breakdown → occurs in heavily doped junction
- occurs with reverse bias voltage less than 6 V
- Temp Coefficient is Negative
- (ii) Avalanche breakdown → Lightly doped junction
- in PN junction diode with reverse voltage greater than 6 V
- Temp. Coefficient is +ve

Symbol!

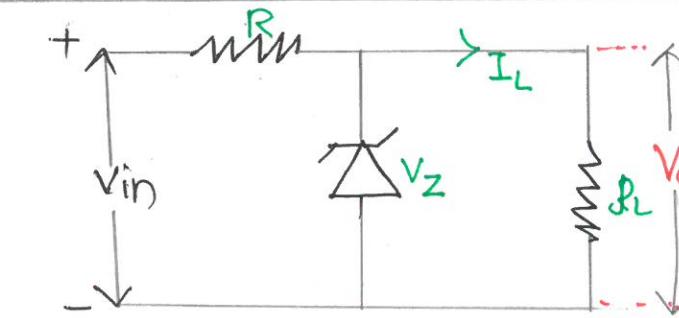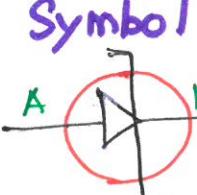

Circuit diagram as a Voltage Regulator

VI Characteristics.

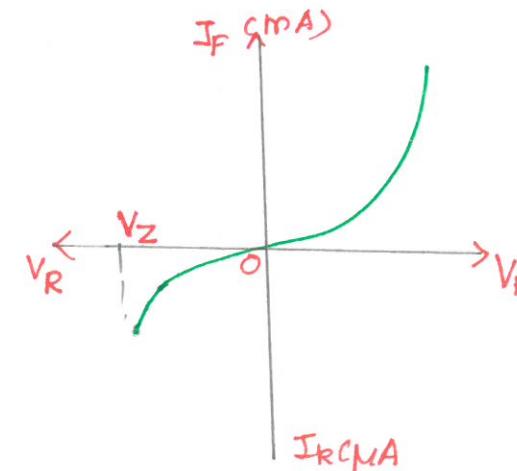

① Zener diode is Same as of PN diode under forward bias condition

② Breakdown occurs under reverse bias.

③ It depends on amount of Doping

④ PHOTO DIODE

① Silicon photo Diode - light sensitive called photo detector - converts Light Signals into Electrical Signals.

Symbol!




Circuit diagram



Characteristics of Photo diode

V-A (VOLTS)

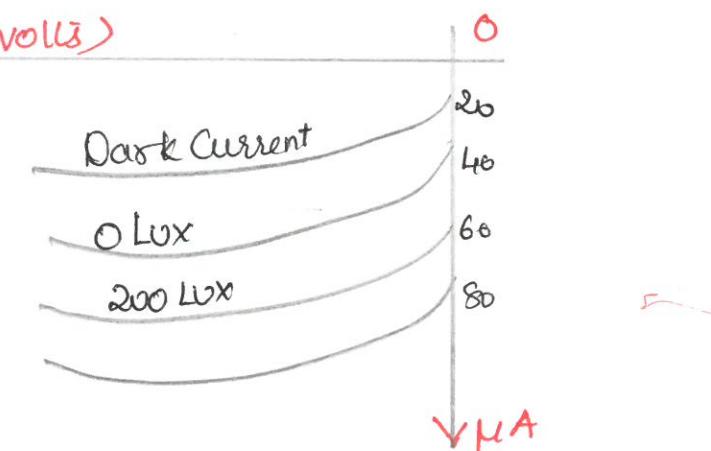

① The Reverse Current increases in direct proportion to the Level of illumination.

② When No Current - minimum Reverse leakage Current - Called dark Current flowing through device

⑤ Applications:-

→ PN Diode :- As Switches, Rectifiers, clippers, clamps.

→ Zenerdiode :- as Voltage Regulators, peak clippers.

→ Photodiode as Light detectors, Encoders and demodulators

Bipolar Junction Transistor


- A BJT is a Three Layer

- Two junction and three terminal device


NPN Transistor

PNP transistor

Circuit Representation and Symbol

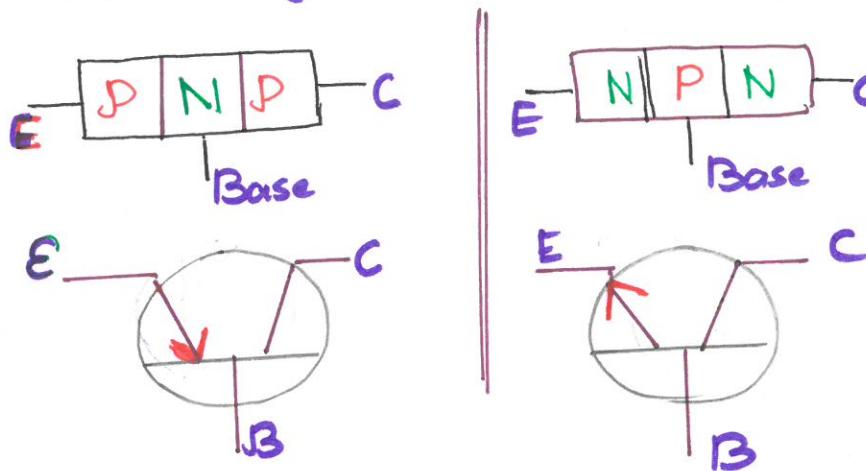

Operation in NPN and PNP Transistor

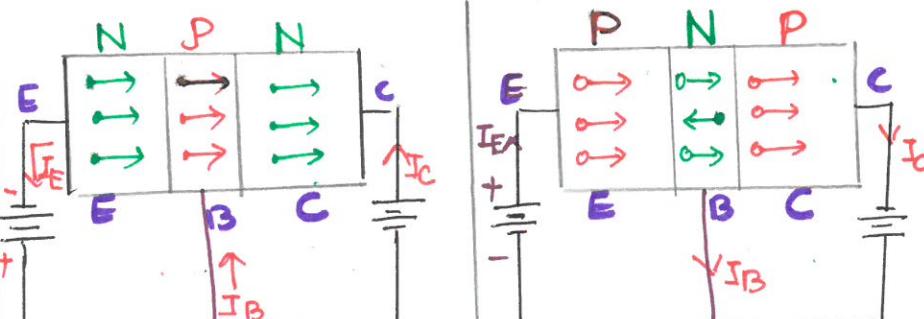

I_C = Collector Current

I_B = Base Current

I_E = Emitter Current

Current Amplification factor

$$\text{In CE Configuration } \beta = \frac{\Delta I_C}{\Delta I_B}$$

$$\text{In CC Configuration } \gamma = \frac{\Delta I_E}{\Delta I_B}$$

$$\alpha = \frac{\beta}{1+\beta} \quad | \quad \beta = \frac{\alpha}{1-\alpha}$$

BJT - Types of Configuration

Common Emitter Configuration (CE)

Common Base Configuration (CB)

Common Collector Configuration (CC)


Common Base:- Also called Grounded Base Configuration

Common Emitter:- Grounded Emitter - Input is Base and Collector is Output

Common Collector:- Grounded collector. Base is Input and Emitter is Output

Common Base Configuration -

Circuit Diagram & Operation

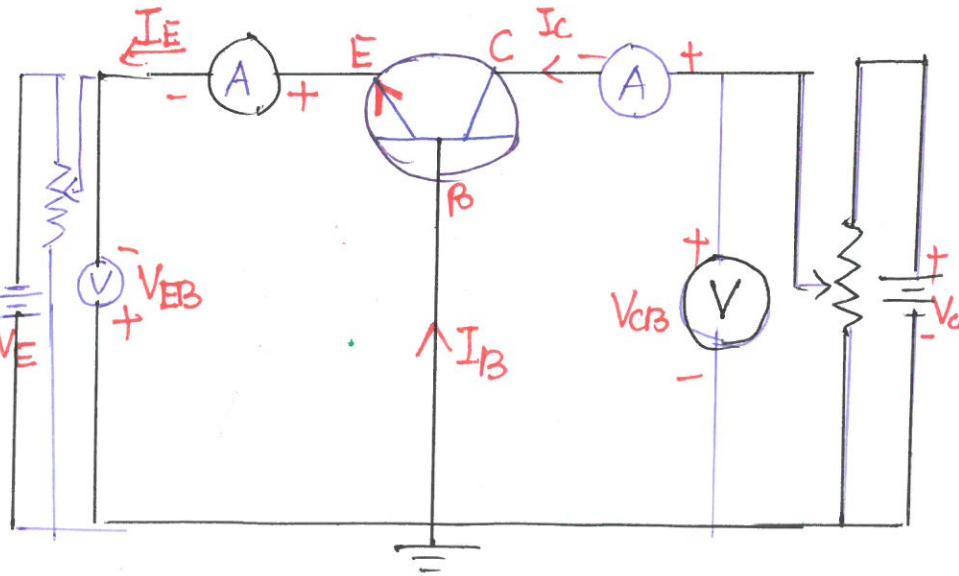

V_E Emitter Voltage


V_{CC} = Collector-Collector Voltage

V_{CB} = Collector-Base Voltage

CB Input Characteristics

I_{ECMA}

3.15
3
2.15
2
1.15
1
0.15

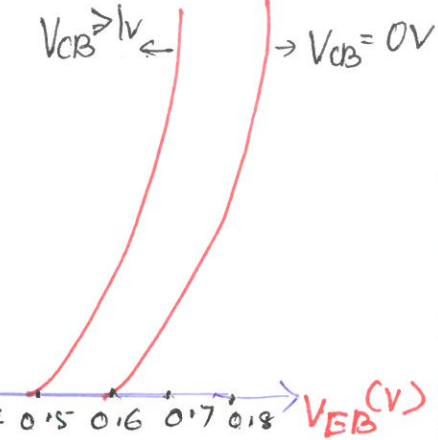

when $V_{CB} = 0$, emitter base junction is forward biased, So I_E increases.

when V_{CB} is increased, V_{EB} as constant, width of base decreases, thus increases I_E .

Output characteristics.

$I_C(mA)$

6
5
4
3
2
1

3mA

2mA

1mA

0mA

To determine output characteristics Emitter Current I_E is constant,

Adjusting Emitter-base voltage V_{EB} , V_{CB} is increased

for a constant value of I_E , I_C is independent of V_{CB} .


Applications:-

- to Amplify weak Signals
- used as a Switch in Digital Circuits
- used in Oscillator Circuits

Common Emitter Configuration.


- ① Input applied between Base & Emitter and output taken from Collector and Emitter.

Input Characteristics:

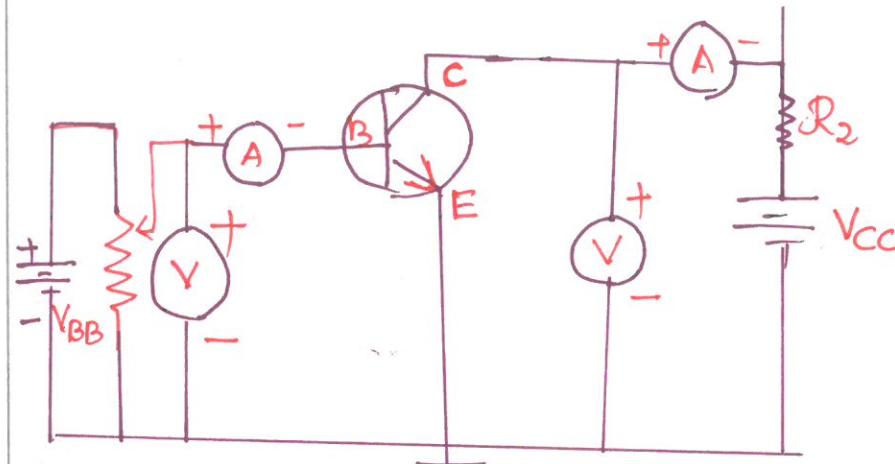

Circuit diagram of CE.

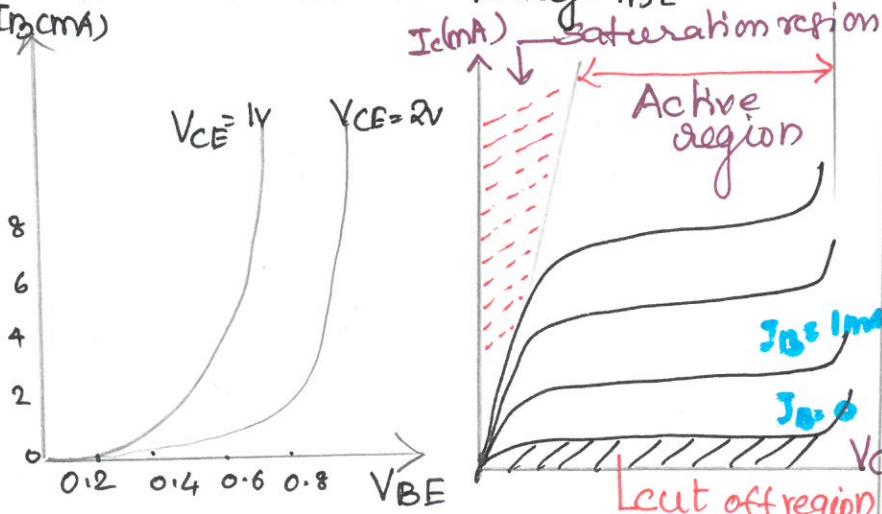- ② Input characteristics between base current $I_{B(A)}$ & Base Emitter Voltage V_{BE}



- ③ Output characteristics is between Collector Current I_c and Collector Emitter Voltage V_{CE}

Input Resistance $R_{in} = \frac{\Delta V_{BF}}{\Delta I_B}$ | constant V_{CE}

Current Gain $\beta = \frac{\Delta I_C}{\Delta I_B}$


characteristics:-

- ① Input Impedance is low (750Ω)
- ② Output resistance is high ($45k\Omega$)
- ③ Voltage Gain is high (about 500)
- ④ Current Gain is high


Application:- used for Audio frequency application

Common Collector Configuration.

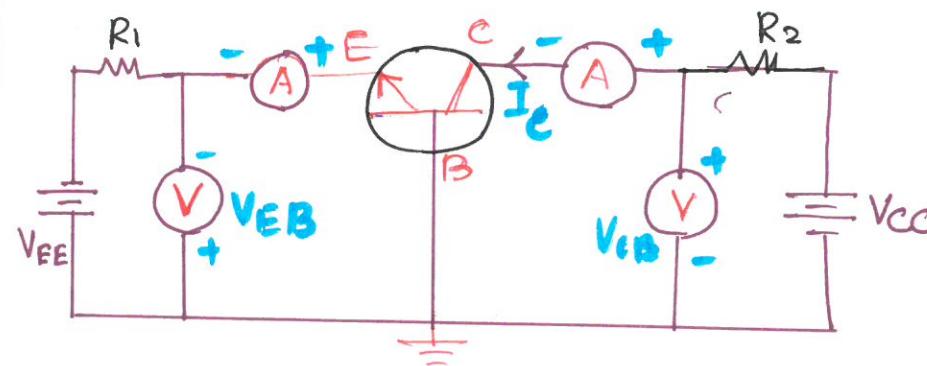To determine the Static characteristics of NPN transistor is shown.




Common Collector Configuration

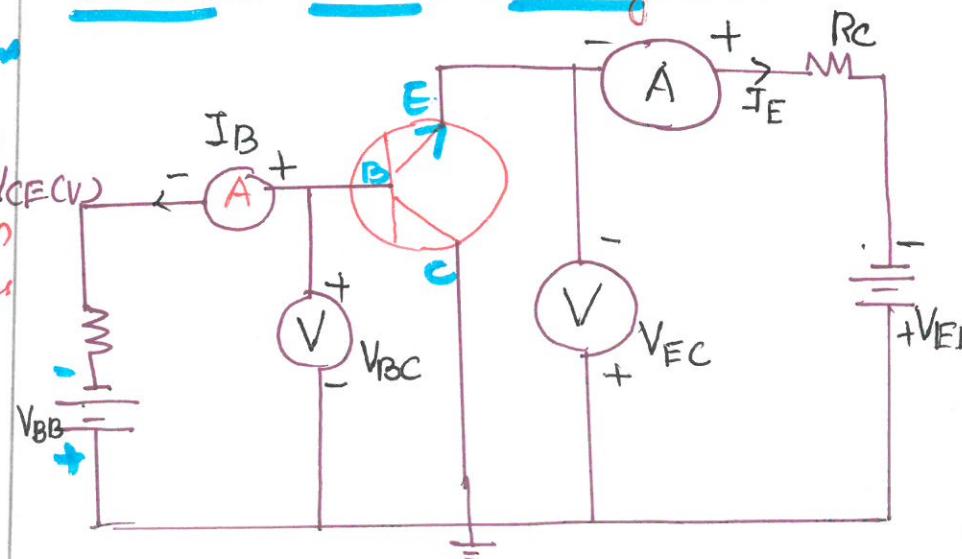

Input characteristics of CC amplifier

$I_E(mA)$

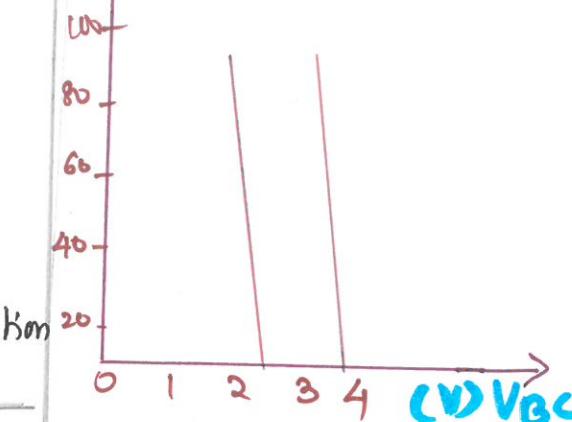

- ① Base current kept Constant, adjusting V_{BC}
- ② Output Current I_E is measured.

$$R_{out} = \frac{\Delta V_{BC}}{\Delta I_E} \mid \text{constant } I_B$$

$$\text{Current Amplification factor } (\gamma) = \frac{\Delta I_E}{\Delta I_B} \mid V_{CE} = \text{const.}$$

Characteristics

- ① Input Impedance is high (about $750k\Omega$)
- ② Output Impedance is Low (about 50Ω)
- ③ Voltage Gain is less than 1
- ④ Current Gain is high.

application:- used for Impedance Matching.

Problem:- calculate I_E in a transistor for which $\beta = 50$ and $I_B = 20\mu A$

$$I_C = \beta I_B = 50 \times 20 \times 10^{-6} = 1 \times 10^{-3} A$$


$$I_E = I_B + I_C = 1 \times 10^{-3} + 20 \times 10^{-6} = 1.02 \times 10^{-3} A$$

$$\alpha = \frac{\Delta I_C}{\Delta I_E} \text{ at const } V_{CB} \quad \beta = \frac{\Delta I_C}{\Delta I_B} \quad \gamma = \frac{\Delta I_E}{\Delta I_B} \mid V_{CE} = \text{const}$$

OPERATIONAL AMPLIFIER

Operational Amplifier is a **Three Terminal** device - consists of two high Impedance inputs


Symbol

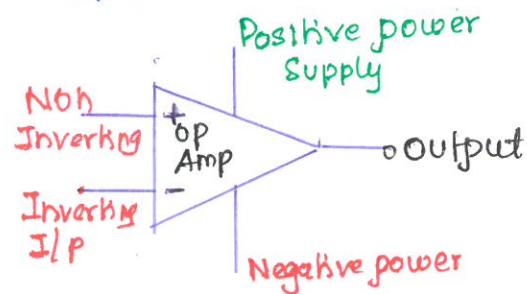

① Is used to Amplify and output the Voltage difference between Two input pins.

Key Characteristics and Parameters


Closed Loop Inverting Amplifier.

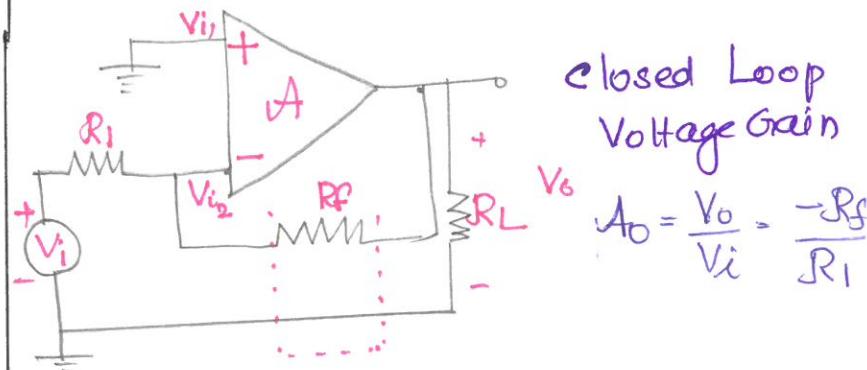

closed Loop Voltage Gain

$$\text{Efficiency } \eta = \frac{\text{dc output power}}{\text{ac input power}}$$

Closed Loop Non-Inverting Amplifier.

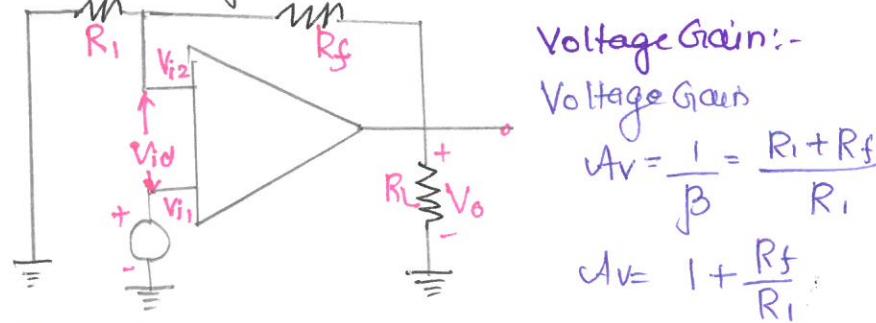

Voltage Gain:-
Voltage Gain
 $A_v = \frac{1}{B} = \frac{R_1 + R_F}{R_1}$

Applications:


- ① performs Summation, Scaling, differentiation, Integration in Analog Computers

Application of Semiconductor devices

DIODE AS A RECTIFIER

① Rectifier used for Converting AC Voltage into Unidirectional Voltage


Half-Wave Rectifier

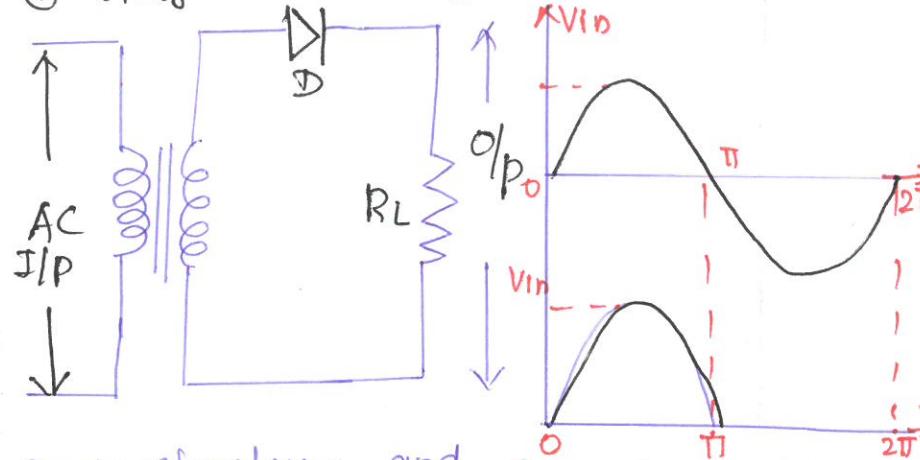

Basic structure and Input/output charac,


$$\text{Efficiency } \eta = \frac{\text{dc output power}}{\text{ac input power}}$$

Zener Diode As a Regulator

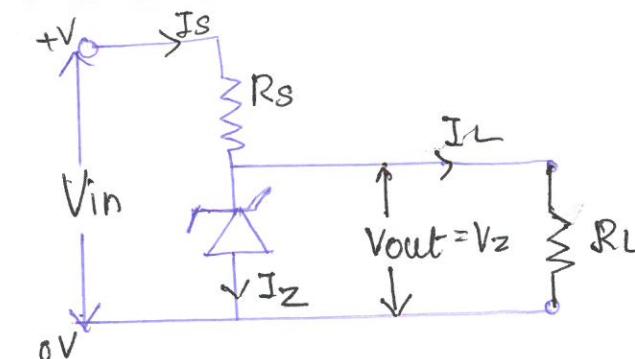


① Designed using a Zener diode to maintain a constant DC output Voltage across the Load.

TRANSISTOR as a Switch

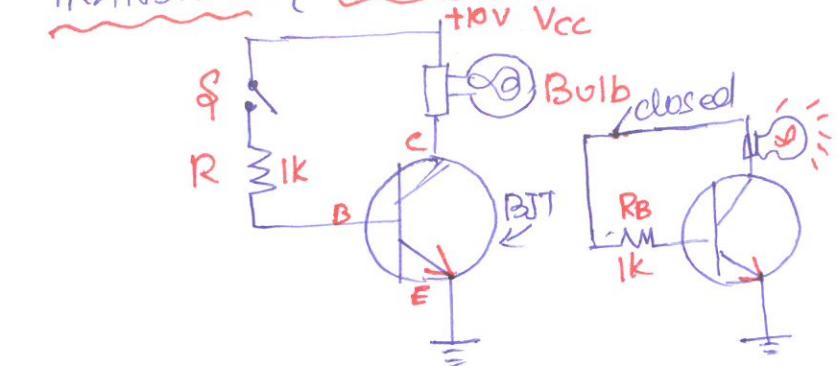

For Switching - BJT is biased to operate in the Saturation or Cut-off Region

Sensitive Intruder Alarm Circuit

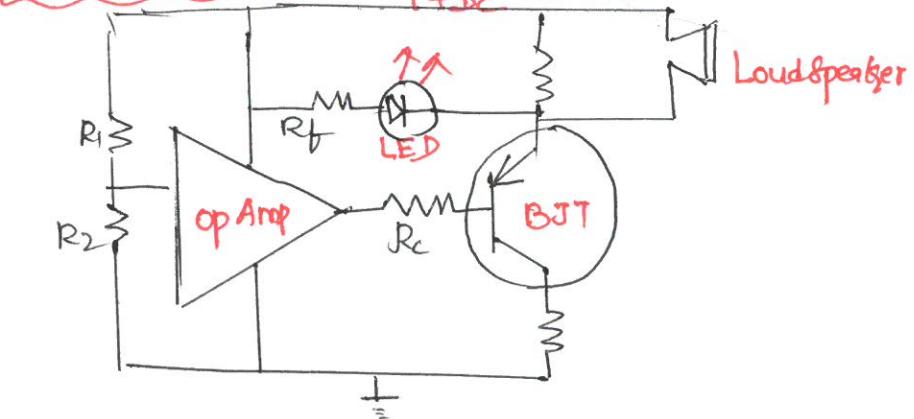

Some other Applications are

- ① Sound operated flip-flop
- ② Sound Pressure Meter
- ③ Infrared Motion Detector Circuit
- ④ Car Subwoofer filter
- ⑤ DIY Headphone Amplifier
- ⑥ Tone Control for Guitar Amplifier
- ⑦ Temperature Deviation Indicator using OpAmp
- ⑧ Operation Amplifier Tester.

Number systems:

- Binary [base 2 (0, 1)]
- Octal [base 8 (0 - 7)]
- Hexadecimal [base 16, (0 - 9), A - F]
- decimal [base 10, (0 - 9)]

Conversions:

Binary to decimal

Eg: 1 0 0 1

$$\begin{array}{r}
 | \\
 | \quad 1 \times 2^0 = 1 \times 1 = 1 \\
 | \\
 0 \times 2^1 = 0 \times 2 = 0 \\
 | \\
 0 \times 2^2 = 0 \times 4 = 0 \\
 | \\
 1 \times 2^3 = 1 \times 8 = 8 \\
 \hline
 9
 \end{array}$$

$1001_2 = 9$

Binary to Octal

Eg: 0 1 1 1 0 0 1 0 1

* group three bits from LSB
* convert to decimal

$$\begin{array}{r}
 | \\
 | \quad 3 \quad 4 \quad 5 \\
 | \\
 4 \quad 5 \quad 6 \\
 \hline
 5
 \end{array}$$

$11100101_2 = 345_8$

Binary to Hexadecimal

Eg: 1 1 1 0 0 1 0 1 1 1 1 1

* group four bits from LSB

$$\begin{array}{r}
 | \\
 | \quad 5 \quad 7 \quad F \\
 | \\
 E \quad 5 \quad 7 \quad F
 \hline
 \end{array}$$

Octal to binary

Eg: 345_8

$$\begin{array}{r}
 | \\
 | \quad 3 \quad 4 \quad 5 \\
 | \\
 0 1 1 \quad 1 0 0 \quad 1 0 1
 \end{array}$$

$$345_8 = 011100101_2$$

Three bit representation of decimal number

Decimal to Octal

Eg: 12345_{10}

$$\begin{array}{r}
 | \\
 | \quad 12345 \\
 | \\
 8 \quad 1543 \rightarrow 7 \\
 | \\
 8 \quad 192 \rightarrow 7 \\
 | \\
 8 \quad 24 \rightarrow 0 \\
 | \\
 3 \quad 0
 \end{array}$$

MSB LSB

$$12345_{10} = 30071_8$$

Octal to Hexadecimal

Eg: 615.25_8

Steps:

Octal \rightarrow three bit representation of each octal digit \rightarrow group 4 bit start from LSB \rightarrow Equivalent Hexadecimal Number

$$\begin{array}{r}
 | \\
 | \quad 615.25 \\
 | \\
 000110001101 \cdot 01010100 \\
 | \quad 1 \quad 8 \quad D \quad 5 \quad 4
 \end{array}$$

$$615.25_8 \rightarrow 18D.54_{16}$$

Octal to decimal

Eg: 3 4 5

$$\begin{array}{r}
 | \\
 | \quad 5 \times 8^0 = 40 \\
 | \\
 4 \times 8^1 = 32 \\
 | \\
 3 \times 8^2 = 192 \\
 \hline
 264
 \end{array}$$

Decimal to Binary

Eg: 24_{10}

$$\begin{array}{r}
 | \\
 | \quad 24 \\
 | \\
 2 \quad 12 - 0 \\
 | \\
 2 \quad 6 - 0 \\
 | \\
 2 \quad 3 - 0 \\
 | \\
 2 \quad 1 - 1
 \end{array}$$

MSB LSB

$$24_{10} = 11000_2$$

Decimal to Hexadecimal

Eg: 725_{10}

$$\begin{array}{r}
 | \\
 | \quad 725 \\
 | \\
 16 \quad 45 \rightarrow 5 \\
 | \\
 16 \quad 13 - D \\
 | \\
 2 \quad 1 - 1
 \end{array}$$

$$725_{10} = 2D5_{16}$$

Hexadecimal to Binary

Eg: A 2 D E₁₆

Four bit representation

$$\begin{array}{r}
 | \\
 | \quad A \quad 2 \quad D \quad E \\
 | \\
 1010 \quad 0010 \quad 1101 \quad 1110
 \end{array}$$

$$A2DE_{16} = 1010001011011110_2$$

Hexadecimal to Octal

Eg: BC66.AF

$$\begin{array}{r}
 | \\
 | \quad B \quad C \quad 6 \quad 6 \quad A \quad F \\
 | \\
 8 \quad 10 \quad 11 \quad 10 \quad 0110 \quad 0110 \quad 1010 \quad 1111 \quad 0 \\
 | \quad 1 \quad 3 \quad 6 \quad 1 \quad 4 \quad 6 \quad 5 \quad 3 \quad 6
 \end{array}$$

$$BC66.AF = 136146.536_{16}$$

Hexadecimal to decimal

Eg: 12A1336

$$\begin{array}{r}
 | \\
 | \quad 16 \\
 | \\
 0 \times 16^0 = 0 \\
 | \\
 15 \times 16^1 = 240 \\
 | \\
 240
 \end{array}$$

(240)₁₀

Problems

Find decimal equivalent of

$$(23.23)_4$$

$$\begin{aligned}
 N &= 2 \times 4^2 + 3 \times 4^1 + 1 \times 4^0 + 2 \times 4^{-1} \\
 3 \times 4^{-2} &= 45.6875_{10}.
 \end{aligned}$$

2) Convert $(12.125)_{10}$ to binary

Integer part

$$\begin{array}{r}
 | \\
 | \quad 2 \quad 1 \quad 2 \\
 | \\
 2 \quad 6 - 0 \\
 | \\
 2 \quad 3 - 0 \\
 | \\
 1 - 1
 \end{array}$$

$$\begin{array}{r}
 | \\
 | \quad 0.125 \times 2 = 0.25 \\
 | \\
 0.25 \times 2 = 0.50 \\
 | \\
 0.50 \times 2 = 1.00
 \end{array}$$

$$\text{Ans. } 1100.001_2$$

3) Convert 658.825 to octal.

$$\begin{array}{r}
 | \\
 | \quad 8 \quad 658 \\
 | \\
 8 \quad 82 - 2 \\
 | \\
 8 \quad 10 - 2 \\
 | \\
 1 - 2
 \end{array}$$

$$\begin{array}{r}
 | \\
 | \quad 0.825 \times 8 = 6.6 \\
 | \\
 0.6 \times 8 = 4.8 \\
 | \\
 0.8 \times 8 = 6.4
 \end{array}$$

$$658.825 = 1222.646_8$$

A) Convert $(101101.1101)_2$ to decimal and hexadecimal.

$$\begin{aligned}
 101101.1101 &= 1 \times 2^5 + 0 \times 2^4 + 1 \times 2^3 + \\
 &\quad 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 + 1 \times 2^{-1} + \\
 &\quad 0 \times 2^{-2} + 1 \times 2^{-3} = 32 + 8 + 4 + 1 + 0.5 + \\
 &\quad 0.25 + 0.0625 = 45.8125.
 \end{aligned}$$

$$\begin{array}{r}
 | \\
 | \quad 2 \quad 0 \quad 1 \quad 1 \quad 0 \quad 1 \quad 1 \quad 1 \quad 0 \\
 | \\
 2 \quad D \quad D
 \end{array}$$

$$0101101.1101_2 = 2DD_{16}$$

LOGIC GATES


GATES

AND GATE

$$Y = A \text{ AND } B \text{ AND } C \dots N$$

$$Y = A \cdot B \cdot C \dots N$$

LOGIC DESIGN

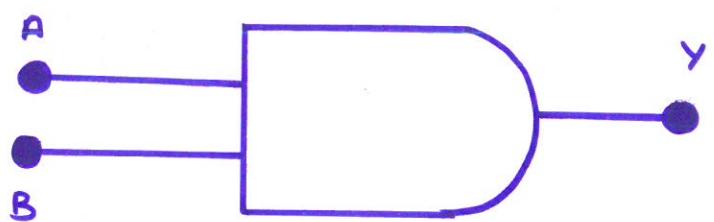


TRUTH TABLE :-

INPUTS		OUTPUTS
A	B	AB
0	0	0
0	1	0
1	0	0
1	1	1

OR GATE


$$Y = A + B + C \dots N$$

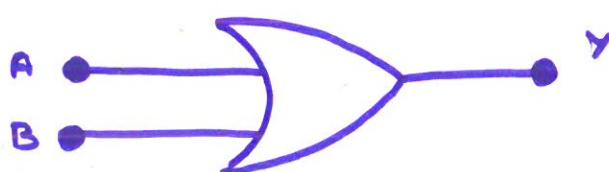

Truth Table :-

INPUT		OUTPUT
A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1


NOT GATE

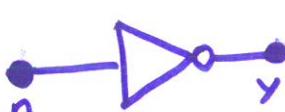


TRUTH TABLE

Input	Output
A	B
0	1
1	0

NAND GATE

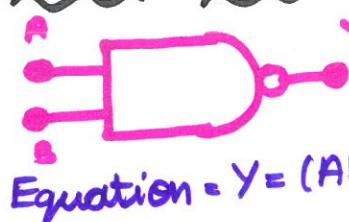

NOR GATE

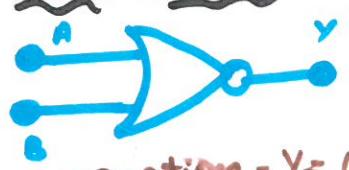


XOR GATE



$$\text{Equation} = Y = A \oplus B$$


XNOR GATE

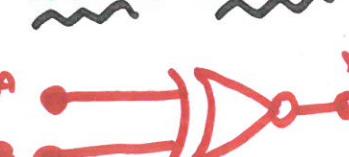


$$\text{Equation} = Y = A \circ B$$

NAND Implementation

NOT GATE USING NAND GATE

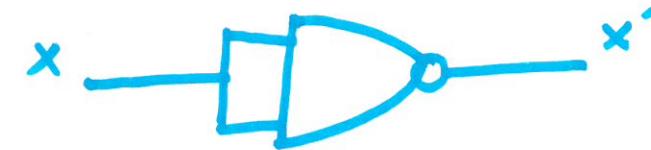


OR USING NAND

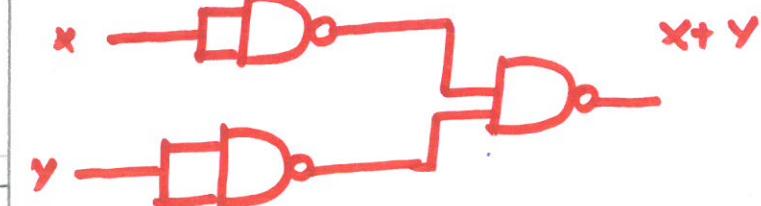


NOR Implementation

inverter using NOR

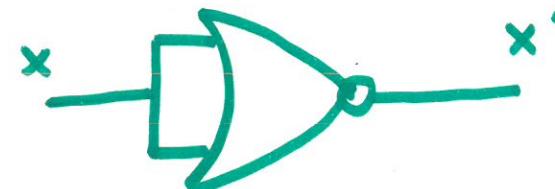


AND using NOR

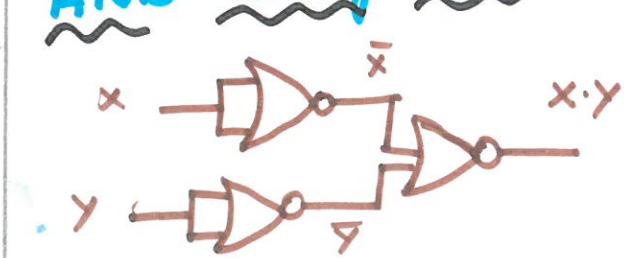


$$\begin{aligned} Y &= \bar{x} + \bar{y} \\ &= \bar{x} \cdot \bar{y} = xy \end{aligned}$$

IMPLEMENTATION


AND USING NAND

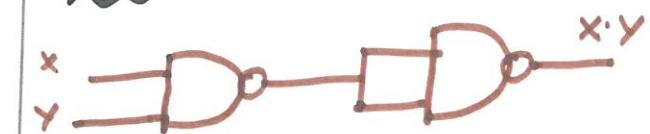


NOR USING NAND

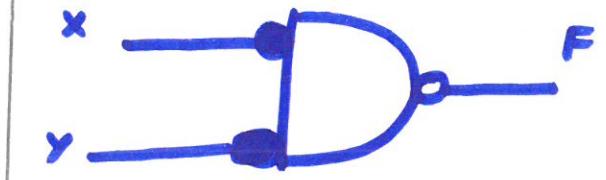

OR USING NOR

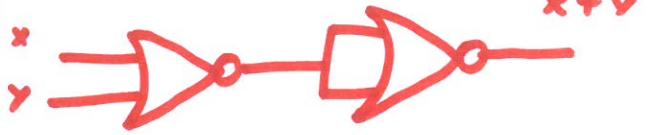

NAND using NOR

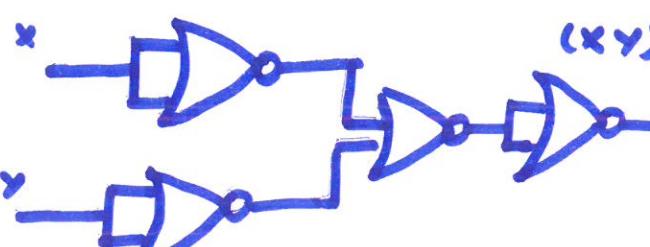

$$\begin{aligned} Y &= \bar{\bar{x}} + \bar{\bar{y}} \\ &= \bar{x} \cdot \bar{y} \end{aligned}$$

Boolean Algebra:

- Simplify the design of logic circuit

- binary variable and logic operations.

Boolean function:

- Algebraic expression consist of binary variable, constants 0 & 1, logic operation symbols.


Simplification of Boolean function

* Using Boolean axioms & laws

* K-Map

* Tabulation Method

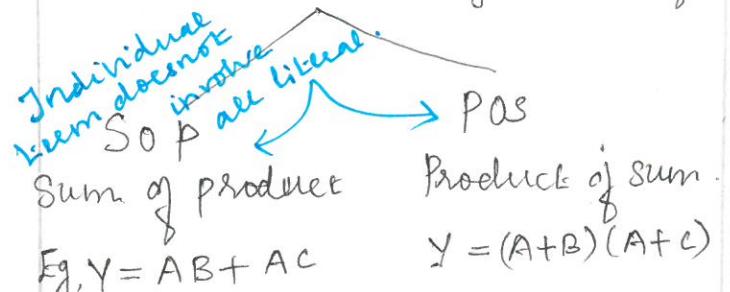The literals, Product terms or Sum terms are arranged in the form



Canonical or Standard form:
- Individual term has all literals

$$\text{Eg: Standard SOP } Y(A, B, C) = ABC + A'BC \\ \text{Standard POS } Y(A, B, C) = (A+B+C)(A+B+C')$$

Postulates and theorems of BA.

1. $x+0 = x$ $x \cdot 1 = x$
2. $x+x' = 1$ $x \cdot x' = 0$
3. $x+x = x$ $x \cdot x = x$
4. $x+1 = 1$ $x \cdot 0 = 0$
5. Involution $(x')' = x$.

6. Commutative $x+y = y+x$

7. Associative $x+(y+z) = (x+y)+z$

8. Distributive $x(y+z) = xy+xz$

$$x(yz) = (xy)(xz)$$

9. De Morgan's law $(x+y)' = x'y'$

$$(xy)' = x'y'$$

10. Absorption $x+xy = x$; $x \cdot (x+y) = x$

Convert given Expression in to Standard form (SOP). *Missing*

$$\text{Eg: } f(A, B, C) = AC + AB + BC. \quad \begin{matrix} B \text{ missing} \\ A \text{ missing} \end{matrix}$$

$$f = AC(B+B') + AB(C+C') + BC(A+A') \\ = ABC + ABC' + ABC + A'BC.$$

Eg: 2: Draw the truth table for $y = a'b + bc$.

* Convert to Canonical form

* Draw truth table by placing 1 against the Minterm. *SOP*

$$y = a'b'c + a'b'c + abc$$

a	b	c	y	$\sum_m(2, 3, 7)$
0	0	0	0	
0	0	1	0	
0	1	0	1	
0	1	1	1	
1	0	0	0	
1	0	1	0	
1	1	0	0	
1	1	1	1	

POS

Eg: 3: Obtain the SOP and POS form

$$F = \sum_m(1, 3) \\ = a'b + ab \quad (\text{SOP}) = b(a+a') = b$$

$$F = \prod_m(0, 2)$$

$$= (a+b)(a'+b) \quad (\text{POS}) \\ = a'b + ab + b = b$$

Boolean function Simplification

Eg 4: Given in SOP form as

$$F = A'BC + A'B'C + C' \\ = A'C(B+B') + C' \\ = A'C + C' = C + CA' \\ F = C + A'$$

Eg: 5 Given in POS form

$$F_2 = (A'+B+c')(A'+B')(C+A)$$

$$F_2 = (A'A' + A'B' + B'A' + BB' + C'A' + C'B') \quad (C+A) \\ = A'A'c + A'B'C + B'A'C + BB'C + C'A'C + \\ C'B'C + A'A'A + A'B'A + B'A'A + \\ B'B'A + C'A'A + C'B'A$$

$$F_2 = A'C + A'B'C$$

Simplification Using K-Map

Karnaugh Map (K-Map)

* graphical Representation of logic

* Reduce logic function quickly & easily.

* Reduces No of gates.

Steps Involved

Step 1: Identify no of input variables

Step 2: Bring given function in Canonical form

Step 3: Draw suitable n' variable

K-Map

One variable K-Map

		0	1	gray	variable
		m ₀	m ₁		
		00	01	10	11
A	/BC	0	1	1	0
A'	ABC	1	0	0	1
		m ₀	m ₁	m ₂	m ₃
		AB	AC	BC	BC

Three Variable

Four Variable K-Map

AB	CD	CD	CD	CD
00	00	01	11	10
01	ABED	ABED	ABCD	ABCD
11	M ₄	M ₅	M ₇	M ₆
10	ABED	ABED	ABCD	ABCD
	M ₁₂	M ₁₃	M ₁₅	M ₁₄
	ABED	ABED	ABCD	ABCD
	M ₈	M ₉	M ₁₁	M ₁₀
	ABED	ABED	ABCD	ABCD

Example 6:

$$Y = A\bar{B}C + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} \\ \begin{matrix} BC \\ 00 \\ 01 \\ 11 \\ 10 \end{matrix} \quad \begin{matrix} \bar{B}C \\ 00 \\ 01 \\ 11 \\ 10 \end{matrix} \quad \begin{matrix} B\bar{C} \\ 00 \\ 01 \\ 11 \\ 10 \end{matrix} \quad \begin{matrix} \bar{B}\bar{C} \\ 00 \\ 01 \\ 11 \\ 10 \end{matrix}$$

$$Y = B + \bar{A}C$$

Example 7: $Y = a'b'c + b'c' + ac$.

Convert to canonical form

$$Y = a'b'c + (a+a')b'c' + a(b+b')c \\ = a'b'c + abc' + a'b'c' + abc + abc' \\ \begin{matrix} 011 \\ 110 \\ 010 \\ 001 \\ 101 \end{matrix}$$

$$Y = \sum_m(2, 3, 5, 6, 7)$$

a'b'c	00	01	11	10
0	m ₀	m ₁	1-m ₃	m ₂
1	m ₄	1	m ₅	m ₆

SOP form.

$$Y = b + ac$$

$$Y = \prod_m(0, 1, 4)$$

a	b	c	a'b	b'c	a'b'c
0	0	0	0	0	0
1	0	0	1	0	0

Pos form.

a	b	c	a'b	b'c	a'b'c
0	0	0	0	0	0
1	0	0	1	0	0

$$Y = (a+b) \cdot (b+c)$$

grouping can be done as pair, quad, octet.

Adders:

Half adder (add 2 bit)


Full adder (add three bit).

Half adder:Truth table:

Inputs		Outputs	
A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


$$\text{Carry} = AB$$

$$\text{Sum} = A \oplus B [AB + \bar{A}\bar{B}]$$

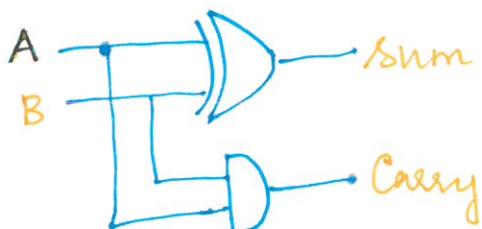Full adder

$$\text{Cout} = AB + AC_{in} + BC_{in}$$

$$\text{Sum} = \bar{A}\bar{B}C_{in} + \bar{A}BC_{in} + A\bar{B}C_{in} + ABC_{in}$$

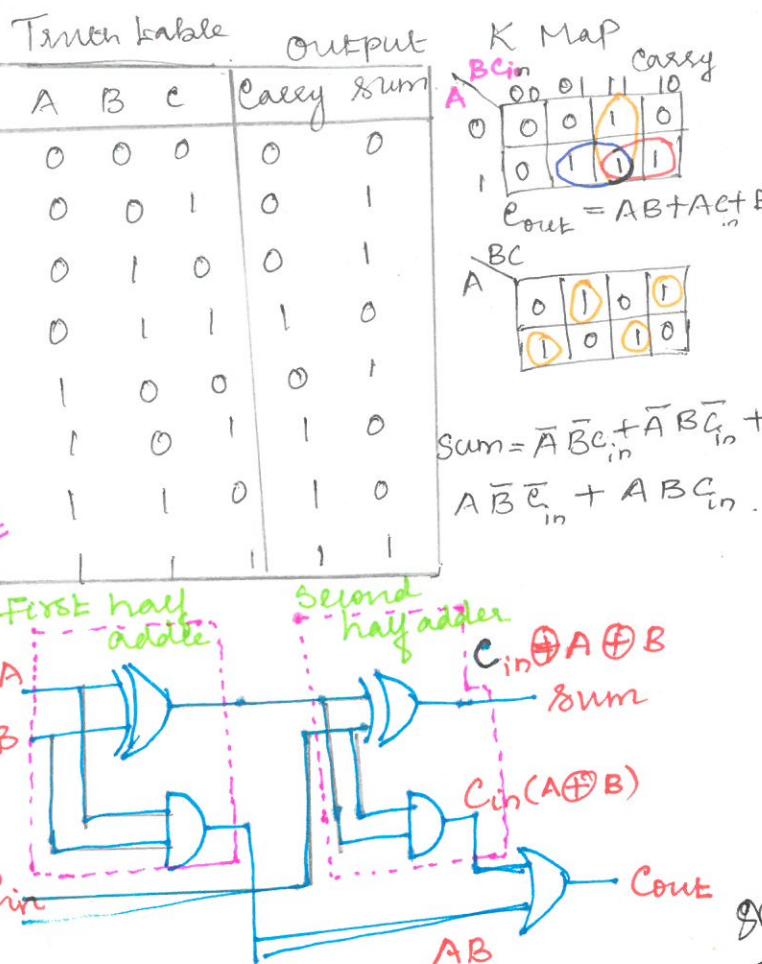Registers:

* group of flip flop - store a word - Registers.

* 1 flip flop store 1 bit, n bit register - n flip flop - store n bits






Shift Registers:

* data moved within register - Clock pulses

* Shifting - arithmetic and logic operation - Microprocessors - Shift registers.

Types of shift register:

1. Serial in serial out Register
2. Serial in parallel out
3. Parallel in serial out
4. Parallel in parallel out

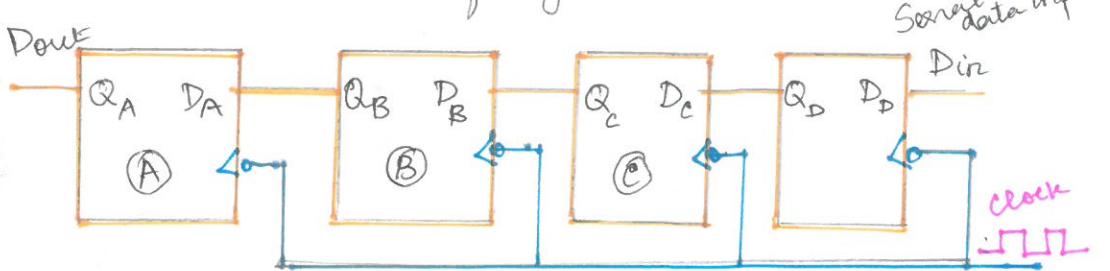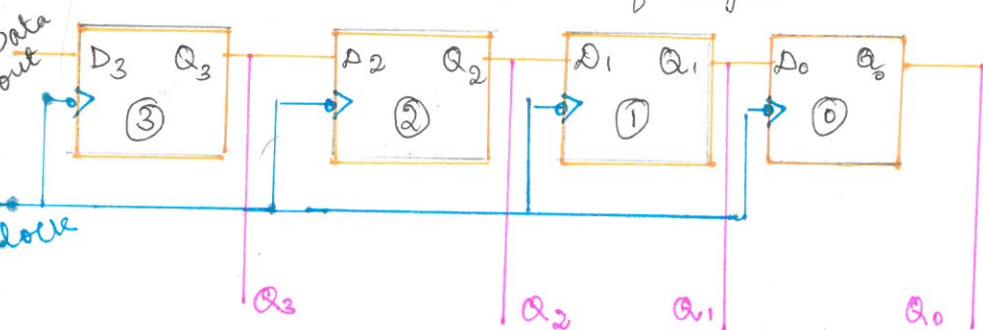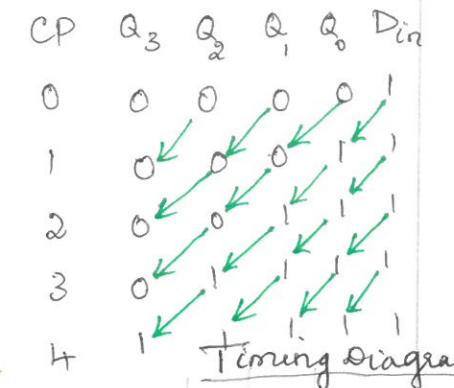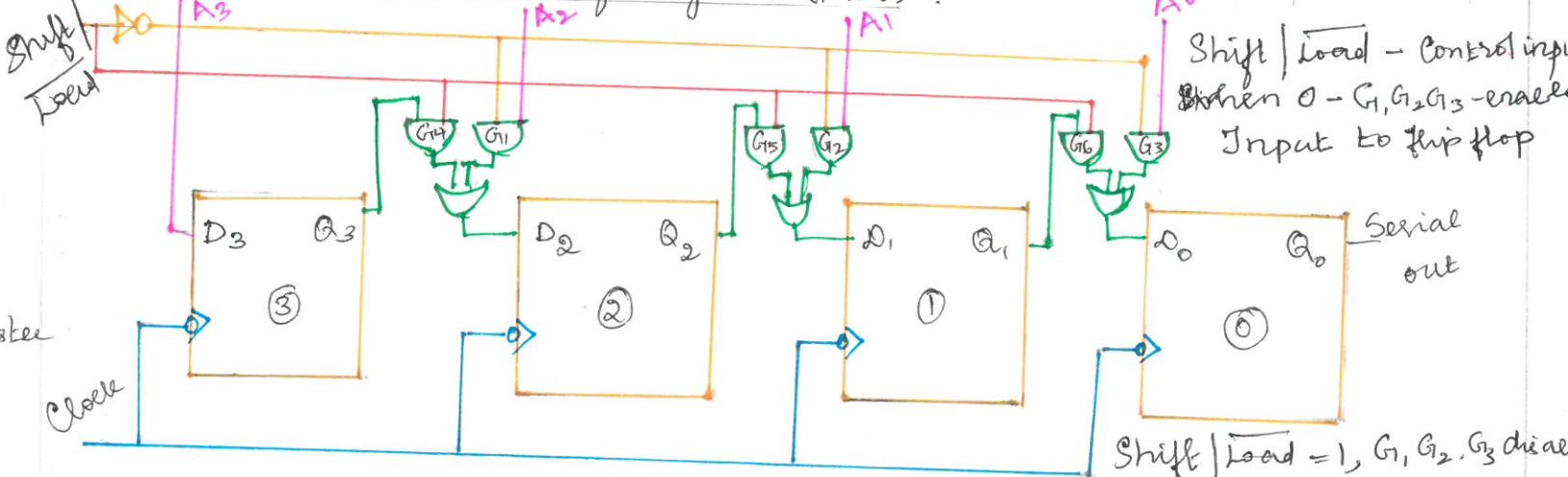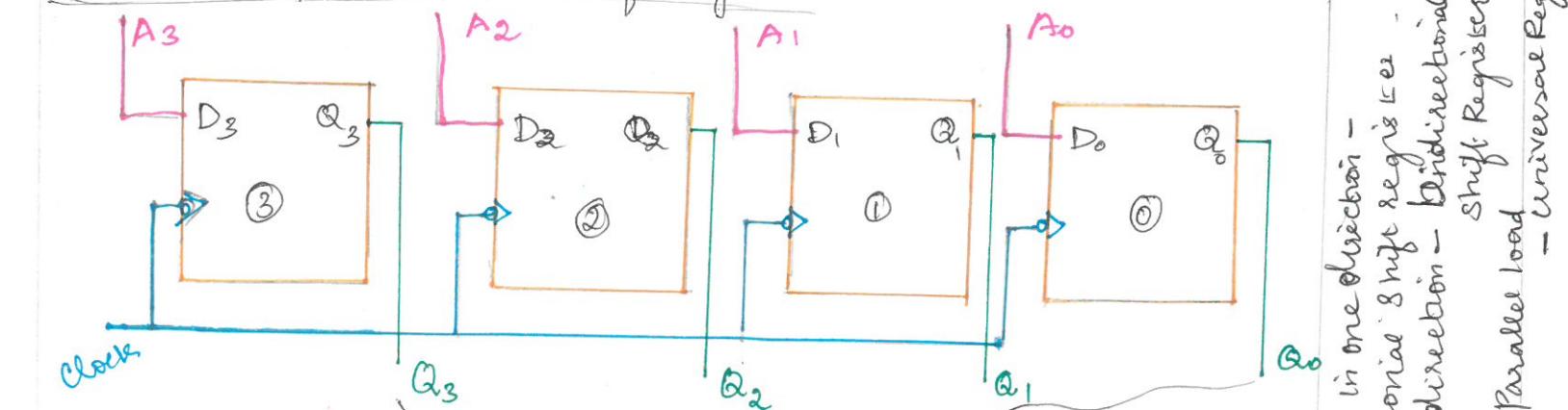Serial in Serial out Shift RegisterSerial in Parallel out (S1PO) Shift RegistersShift register operationParallel in Serial out Shift Registers (PISO)Parallel in parallel out Shift RegisterParallel data output

- Simultaneous entry of all data bit

bit appears on parallel outputs simultaneously

Applications :- Delay line, Pseudo Random Binary sequence generator, Sequence generator, sequence detector, Serial in parallel converter etc

Register Shift in one direction - Uni-directional 8 bit register
Shift both direction - Bidirectional shift register
both Shift & Parallel load - Universal register

Digital Circuits

- Combinational Ckt
- Sequential ckt.


Combinational Circuit:

- * consist logic gates - output depends on present combination of input

- * operation specified by Boolean function.
Eg, Adder, Subtractor, encoder, mux etc

Sequential Circuit:

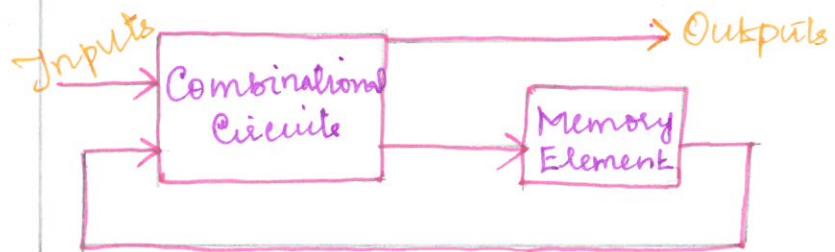- * employ storage elements & logic gates
- * output depend on present and past value of inputs.



- Storage elements ~~are~~ store binary info -
flip flops.


Flip flops

- * Storage element - Clocked Seq. Ckt
- * store one bit of information.

Types of flip flop

1. D flip flop
2. SR flip flop
3. JK flip flop
4. T flip flop

Triggering
level
edge.

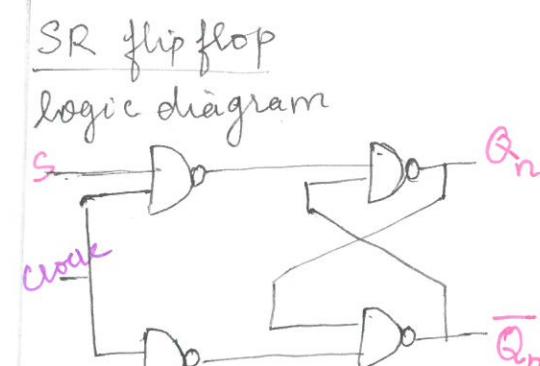

Truth Table


S	R	Q_{n+1}	State
0	0	Q_n	No change
0	1	0	Reset
1	0	1	Set
1	1	X	Undefined

$$Q_{n+1} = S + \bar{R} Q_n$$

Excitation Table

Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

JK flip flop

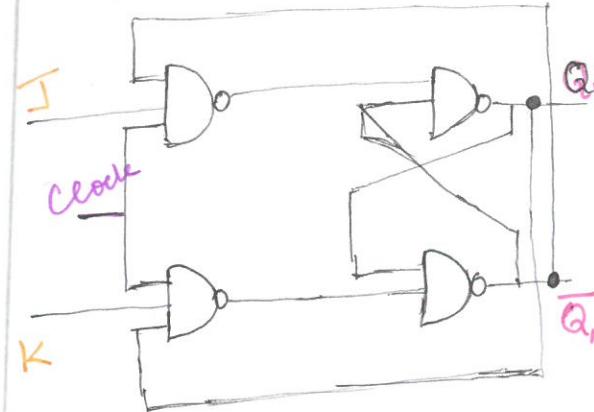


J	K	Q_{n+1}	State
0	0	Q_n	No change
0	1	0	Reset
1	0	1	Set
1	1	\bar{Q}_n	Toggle

Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

$$Q_{n+1} = \bar{J}\bar{Q}_n + \bar{K}Q_n$$

T flip flop

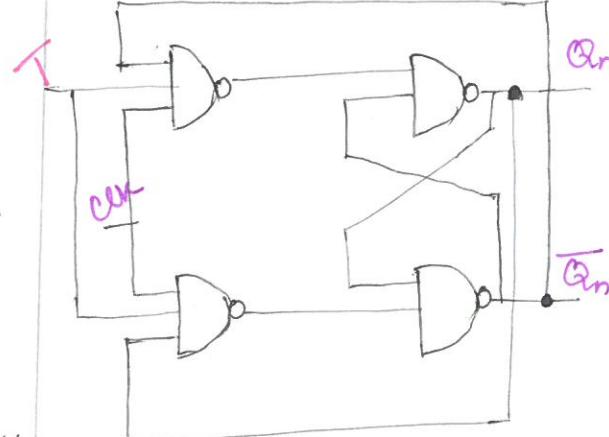


T	Q_{n+1}	State
0	Q_n	No change
0	\bar{Q}_n	Toggle
1	\bar{Q}_n	Toggle
1	Q_n	Toggle

$$Q_{n+1} = T\bar{Q}_n + \bar{T}Q_n$$

T → Toggle

Master Slave flip flop

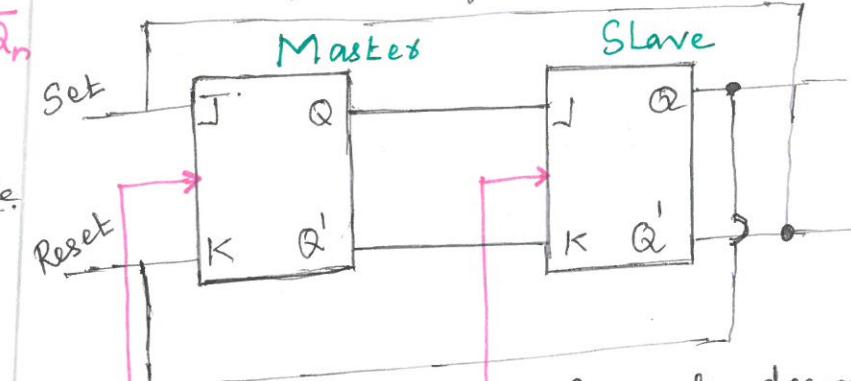- * Pulse triggered flip flop
- * Master triggered by external clock pulse train
- * output from master connected to input of slave flip flop



* Can also be designed using D FF & SR FF also

Why Master Slave - Race around condition

- * In JK FF, when J = K = 1, output toggles.
- * Initially Q = 0, J = K = 1, after Δt , output change to Q = 1. After time Δt , the output changes to Q = 0.
- * Toggling continues until flip flop is enabled and $J = K = 1$.

- * At the end of Clock pulse, the flip flop is disabled. Value of Q is uncertain - race around condition.

Clock pulse width

- * This occurs when $t_p \geq \Delta t$.

- * $t_p < \Delta t$, avoid race around condition.

- * Most practical method - Master-Slave Configuration

Operation: $J = 1; K = 0$ Master sets on positive clock.

Output - high \rightarrow J input to Slave,
Negative clock - Slave sets.

$J = 0, K = 1$, Master resets on positive clock, output - high \rightarrow K input of Slave, Negative clock - Slave resets.

$J = K = 1$, Master toggles on positive clock, Slave copies the output of Master on negative clock.

$J = k = 0$, output of Master remains same in + & - clock.

Counter:

- Register capable of counting the number of clock pulse.
- n-bit Counter - n flip flop - 2^n distinct states of outputs.
- Reaching Maximum Count - reset to zero on next clock pulse

Types

→ Synchronous Counter
[flip flop in counter triggered at same time]

→ Asynchronous Counter


[Output of each flip flop → Clock input of next flip flop]

Modulus of Counter:

- Total Number of Counts or Stable States
- 4 Stage Counter - Mod 16 → 0000_2 to 1111_2 .
- Modulo - Count capability

Mod 10 Counter State diagram:

Ex: 1

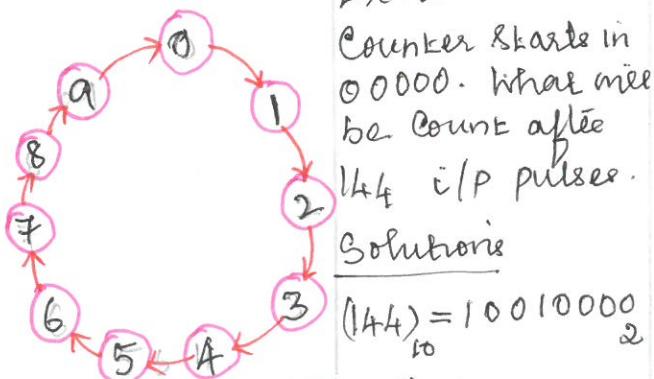

Since 5 bit it resets after $2^5 = 32$ clock pulse
Counter resets four times and then it counts remaining 16 clock pulse. Count will be $(1000)_2$ 16 in decimal.

Design of Counter

1. Identify the No of variables
2. Construct State Table
3. Get the state equation
4. Construct Ekt using flip flop.


Asynchronous Up Counter (Ripple).

3 Stage Counter - 3 flip flops, \rightarrow K flip flop.

High

Low

Domestic Wiring

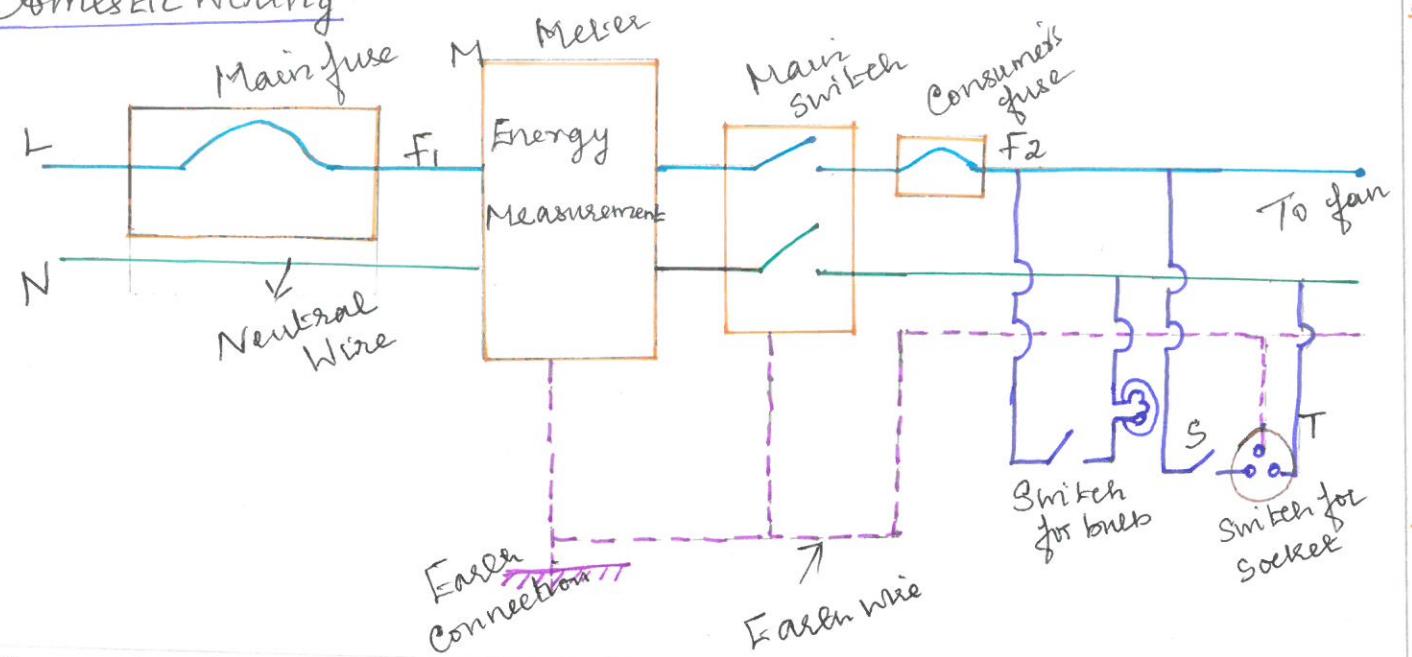

Domestic wiring:

- deals with power distribution inside house, 230V, 1 phase or 400V, 3 phase
- Electricity generated at power station → home - transmitted by parallel wires [live (L), Neutral, Earth].
- Residential loads - connected in parallel. Voltage remains same through loads, if a circuit fails, it does not affect others.
- House - two separate circuit
 1. Lighting Ckt with 5A fuse
 2. Power circuit with 15A fuse

Components of wiring:


1. Switches
2. Lamp holders
3. Ceiling Roses
4. Mounting Blocks
5. Socket outlets
6. Plug
7. Main Switch
8. Distribution Fuse boards
9. Accessories used.
10. Two way switch

Types of Wiring

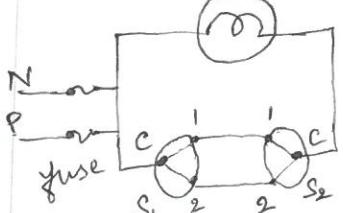
1. Cleat wiring
2. Wooden Casing Capping
3. TRS Wiring
4. Conduit wiring
5. Wiring Circuits
 - a) stair & case wiring
 - b) fluorescent wiring

Staircase Wiring

- single lamp controlled from both plates.
- 2, two way switches need.



Fluorescent tube

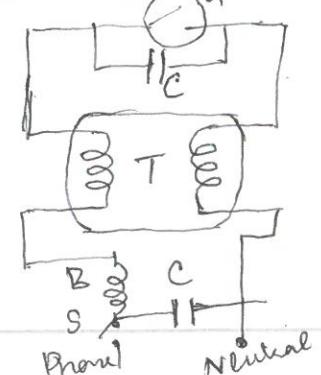


Earthing

- Connected to the Mass of the Earth
- Safe discharge of electric current due to leakage, faults etc.
- Use low resistance wires.
- Before electric supply lines OR apparatus are energized, all earth system - tested for electrical resistance - efficient earthing

Earthing through a GI pipe

- * GI pipe is used as earth electrode
- * Size of pipe - Current carried, type of soil electrode buried.
- * Ordinary Soil - Earth electrode
 - 2m long, 38mm diameter
 - 1.37m long, 51mm dia.


- * dry & rocky soil, length - 2.75mm

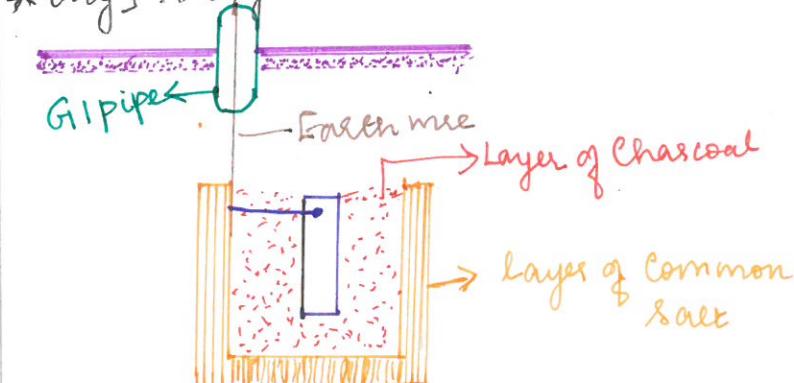

Earthing through a plate

GI Plate - 0.3 x 0.3m dimensions
6.35mm thick

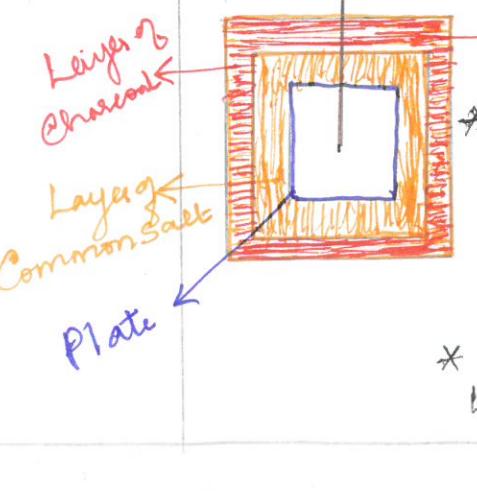Copper plate - 0.3 x 0.3m dimensions
3.2mm thick



- * Plates buried to a depth of not less than 2m in moist close proximity to water tap, water pipe or water drain.
- * plate covered by common salt 30mm.

Types of Earthing

a) Neutral Earthing


Neutral - Earth System earthing System with star winding generator, transformer, motor etc.

b) Equipment Earthing:

- * Electrical Equipment.
- * Non Current Carrying part of equipment
- Connected to earth

Importance of Earthing:

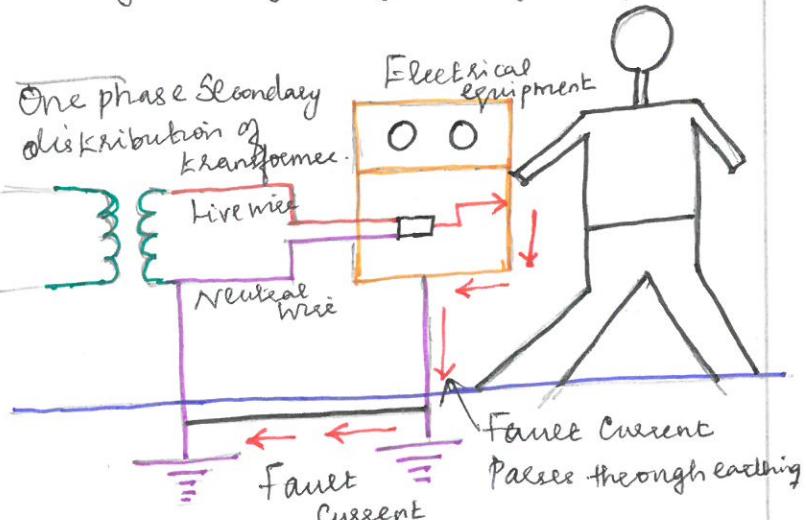- Protects from shock circuit current
- Provide easiest path to flow short circuit current after failure of insulation
- Protect apparatus and personal from high voltage surge & lightning discharge.



- * Fault current - Fault current from equipment flows through earthing system to earth.

- * Earth mat - Conductors rise to the surface = resistance of earth mat X ground fault.

- * Contacting assembly - earthing

- * Metallic Conductors Connect part of installation with earthing - Electrical Connection

- * Earthing and Earthing Connection - Earthing system.

Types of Batteries and Characteristics of Batteries

(24)

Types of Batteries:

Def:

- * Collection of one or more cells.
- * Undergo chemical reaction
- * Create flow of electrons.

Components:

- 1) Cathode (Negative Electrode)
- 2) Anode (Positive Electrode)
- 3) Electrolytes

Types of Batteries:

- 1) Primary Batteries
- 2) Secondary Batteries

Primary Batteries:

- * Cannot be recharged.
- * Made of electrochemical cells.
- * Electrochemical reaction cannot be reversed.
- * Range: coin cells to AA Batteries
- * These batteries always have high specific energy.

Applications:

- * Used in standalone apps, where charging is impractical and impossible.
- * Pace makers, Animal trackers, Wrist watches, Children toys.

Secondary Batteries:

- * Chemical reaction can be reversed.
- * Can be recharged.
- * Used in high drain applications.
(eg) Mobile phones
Electric Vehicles

Types of Secondary Batteries:

- 1) Lithium-ion (Li-ion)
- 2) Nickel Cadmium (Ni-Cd)
- 3) Nickel - Metal hydride (Ni-MH)
- 4) Lead - Acid.

1) Lithium-ion (Li-ion)

- * Lightweight in nature.
- * Used in mobile phones

2) Nickel Cadmium (Ni-Cd)

- * Hold the charge when not in use.
- * Have good life cycle
- * Used in electric vehicles, aircraft starting batteries.

3) Nickel - Metal hydride (Ni-MH)

- * Chemical reaction at the positive electrode is same as (Ni-Cd)
- * In negative electrode Hydrogen absorbing alloy is used instead Cd.

4) Lead Acid:

- * Used in heavy duty applications
- * Low cost.
- * Used in non portable applications.
(eg) Solar Panel Energy Storage.

Characteristics of Battery:

1. Types:

- * Classified based on chemical composition, size, form factor and uses.

2. Voltage:

- * Actual voltage is lower than theoretical voltage (IR drop, and polarization - reason)
- * Depend on load current, internal impedance

3) Discharge Curve:

- * It is plot
- * Voltage Vs Percentage of Capacity discharged.

4) Capacity:

$$Q = x n F$$

$x \rightarrow$ no. of moles of reaction
 $n \rightarrow$ no. of electrons transfer per mole of reaction.

$F \rightarrow$ Faraday's Constant.

$Q \rightarrow$ Quantity of electricity.

5) Energy Density:

Energy derived per unit volume of the weight of the cell.

6) Specific Energy Density:

- * Energy derived from unit weight of the cell.

7) Power Density:

- * Power derived from unit weight of the cell (W/kg)

8) Temperature dependence:

- * Rate of reaction will be temperature dependent.

- * Low temperatures, higher internal resistance.

9) Service life:

- * No. of charge/recharge cycles before its capacity falls to 80%.
- * 500 to 1200 cycles.

10) Physical Requirements:

- * Includes geometry
- * Size, weight, shape and location of the terminals.

11) Cycle life:

- * No. of discharge/charge cycles before its capacity falls to 80%

12) Cost:

- * Cost of battery, cost of charge, cost of maintenance.


Elementary Calculations for Energy Consumption:

Energy Consumption = use of Power or energy of a system
Giga joule / year, watts.

Energy Consumption formula
 $E = \frac{P \times t}{1000}$


$E \rightarrow$ Energy in Kilowatt hours.
 $P \rightarrow$ Power in Watts.
 $t \rightarrow$ hours.

Power factor

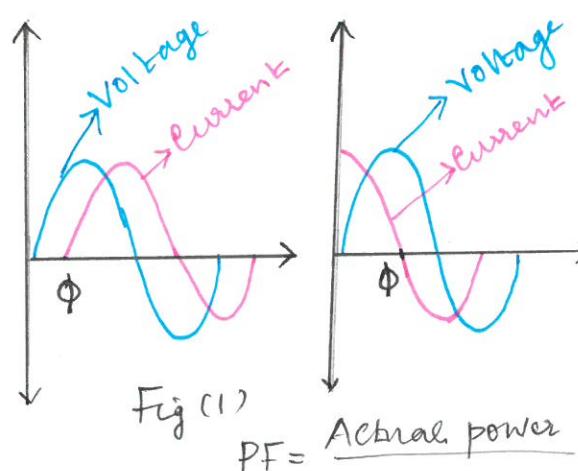

$$PF = \frac{\text{Actual power}}{\text{Apparent power}}$$

Fig (2)

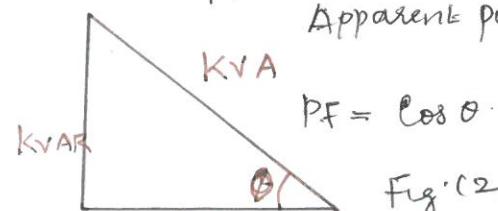

$$\text{Power factor} = \frac{\text{Real power}}{\text{Apparent power}}$$

$$PF = \cos \theta$$

$$KVA = \frac{KW}{\cos \theta}$$

$$KVAR = \frac{KW}{\tan \theta}$$

$$True / Real power = KW$$

$$(Fig 3)$$

Power - Capacity to do work

Electrical power = Electrical energy transferred from one form to other / unit time

Power = Voltage drop across the element \times Current flowing through it.

DC circuit with DC voltage source - Inductor & Capacitor - Short Ckt & open Ckt - Steady state.

AC Circuit - Inductor and Capacitor - Impedance

$$X_L = 2\pi fL, X_C = \frac{1}{2\pi fC}$$

Inductor - store electrical energy - Magnetic energy; Capacitor - electrostatic energy. Neither dissipative - Phase shift V & I.

Ckt with resistor, inductor and capacitor - Phase difference b/w Source Voltage & I - Cosine of phase difference - Power factor
 $-1 < \cos \phi < 1$

Total power = Voltage across element \times Current through the element
Apparent power unit VA \rightarrow S

Active power - fraction of electric power does our useful work (P) watts.

Reactive power - does no useful work \rightarrow requires reactive work to be done. Q.

Total electrical power unit = VAR

Reactive power oscillates between source and load.

Ref fig (3) $S^2 = P^2 + Q^2$

Power factor improvement:

$$\cos \phi = \frac{\text{Active power}}{\text{Apparent power}}$$

Need for power factor improvement:

* Electrical Current $\propto \frac{1}{\cos \phi}$

* Higher the Power factor, lower the Current flow.

* Small current requires less cross section area of conductor - save conductor & money.

* Poor power factor increases current flow
- Copper loss increases - Poor voltage regulation.

* KVA rating reduced

$$KVA = \frac{KW}{\cos \phi}$$

Methods to Improve PF:

* Capacitor bank

- Most loads are inductive
- Capacitor connected in parallel to reduce phase difference.

* Synchronous Condenser

Compensate leading or lagging power factor

Absorbs or supply reactive power to the line.

* Phase Advance

Provides exciting ampere turns to produce required flux.

Power factor Calculation:

$$\cos \phi = \frac{P}{VI} = \frac{\text{Wattmeter reading}}{\text{Voltmeter reading} \times \text{Ammeter reading}}$$

General Safety requirements as per IE rules

- All power supply lines & apparatus with
 - * Proper power rating
 - * Proper insulation

- Supplies to ensure safety of Apparatus & wires

- Switches on live conductors

- No cut out on Neutral wire

- Code of practice for wiring.

- Energy not to be supplied.

Problem 1:

Compute the energy consumption in a system that consumes 190W of power and works for 3 hrs / day.

Soln $P = 190 \text{ W}, \text{ total hours} = 3$.

$$\text{Energy consumption } E = \frac{PE}{1000}$$

$$E = \frac{190 \times 3 \times 60 \times 60}{1000}$$

$$E = 2052 \text{ kWh}$$


Problem 2: A toy car consumes 500watts of power if it works for 2hr / day. Calculate energy consumption.

$$P = 500 \text{ W}, \text{ total hours} = 2 \text{ hrs}$$

$$E = \frac{PE}{1000} = \frac{500 \times 2 \times 60 \times 60}{1000}$$



$$= 3600 \text{ Wh}$$

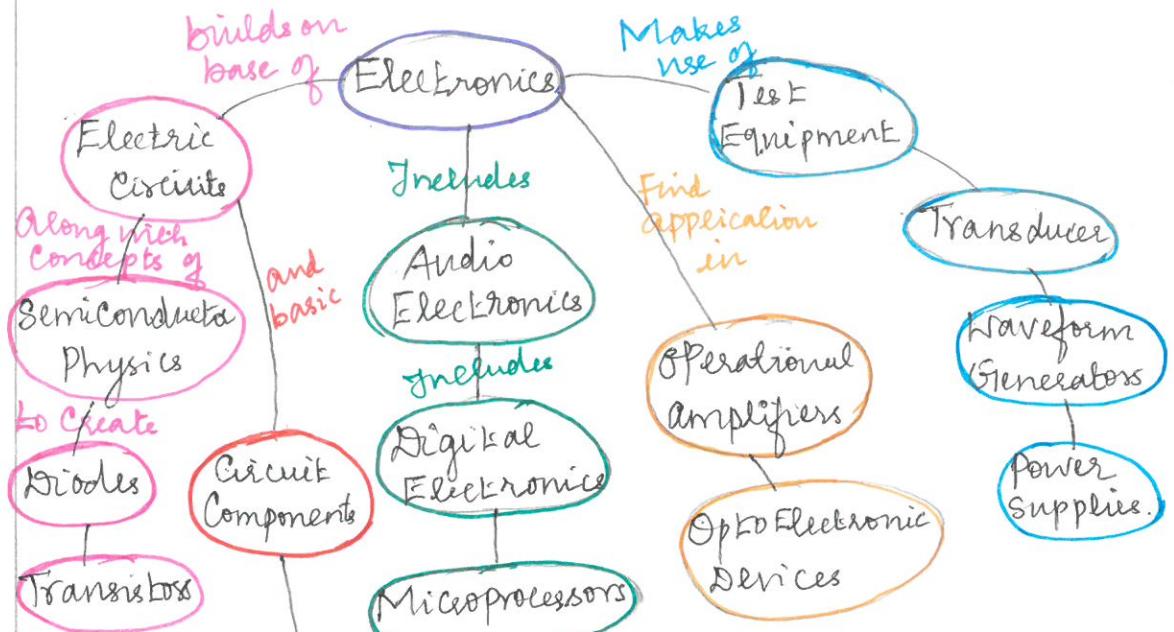APPLICATIONS & FUTURE SCOPE of ELECTRICAL and ELECTRONICS.



Diode Application

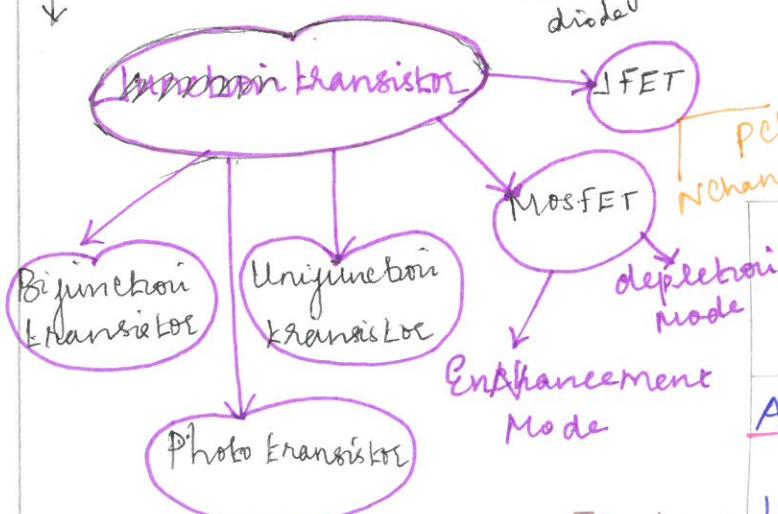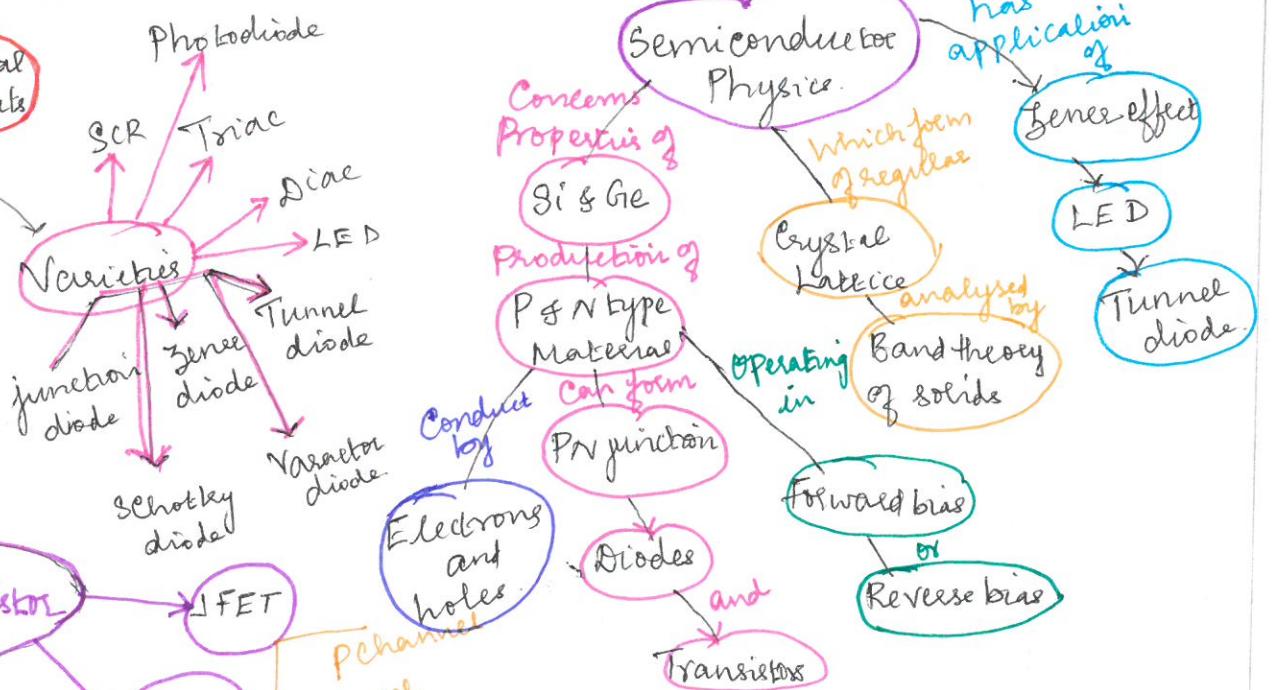- Rectification
- AM detector
- FM detector
- Voltage doublers






Core areas of Industrial Electronics

1. Power electronics
2. Factory automation
3. Mechatronics
4. Intelligent systems
5. Internet based applications

Application of flip flops

Application of Electronics

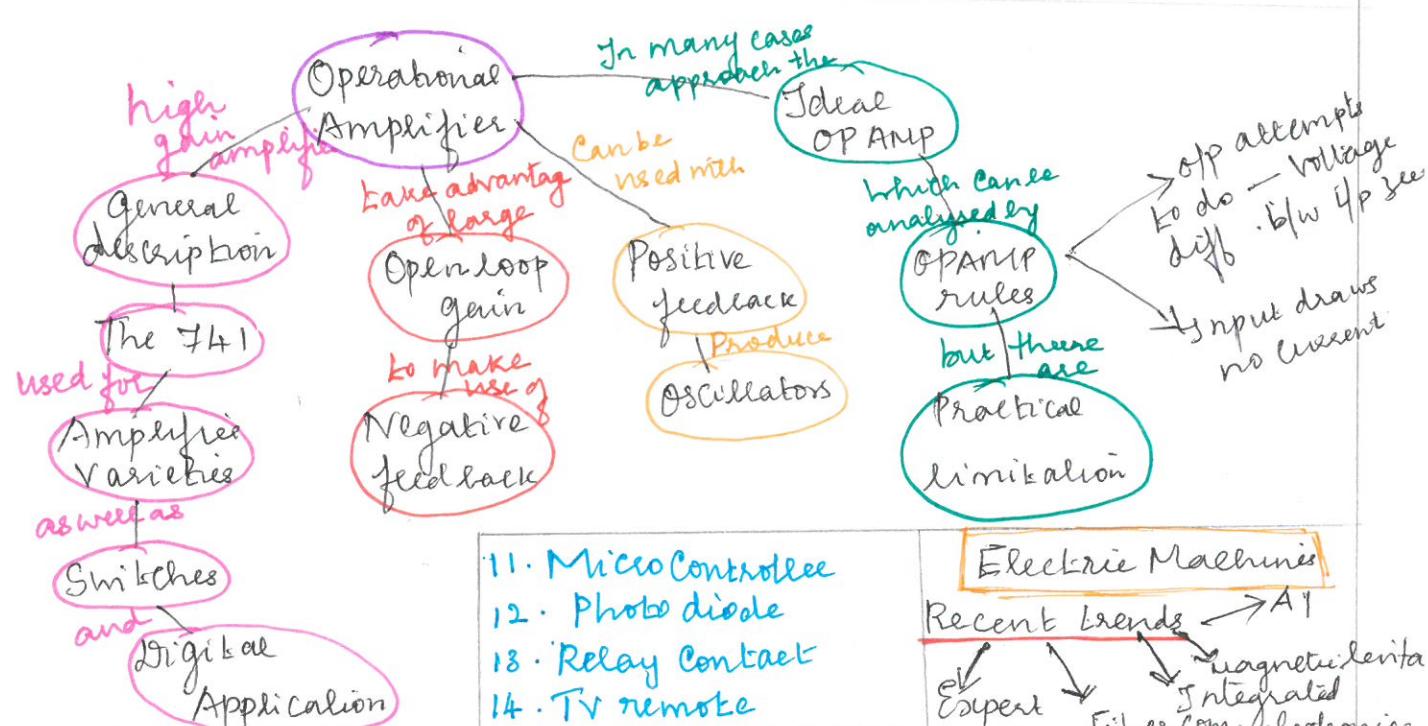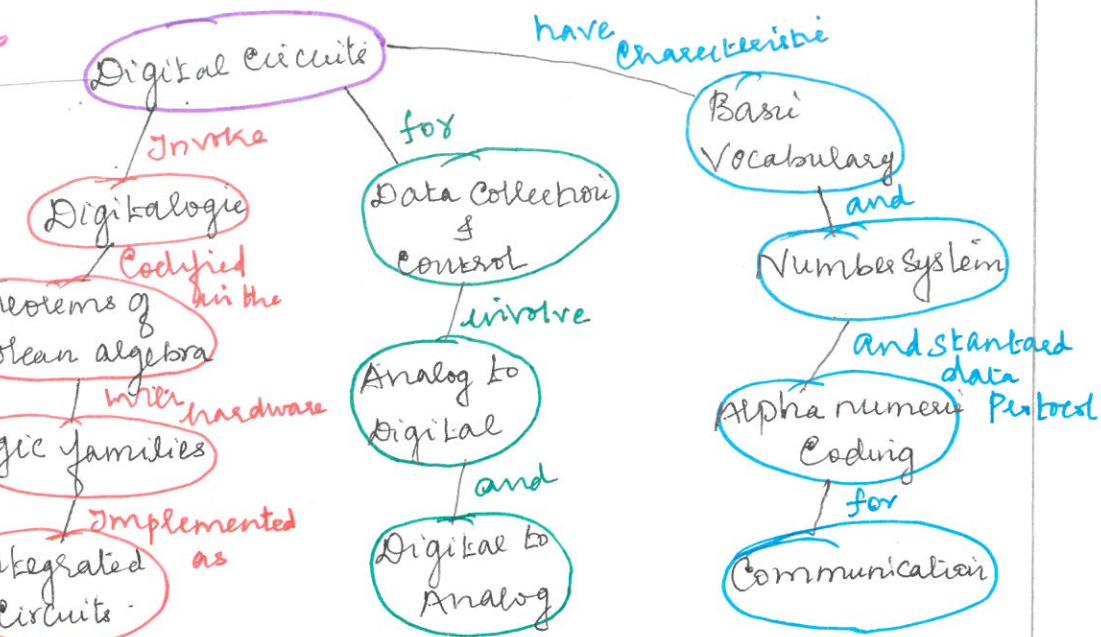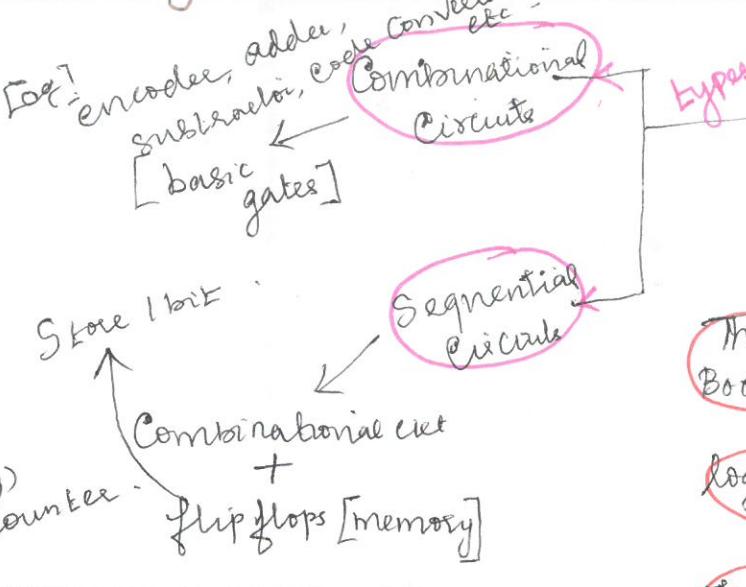


11. Micro Controller
12. Photo diode
13. Relay Contact
14. TV remote
15. Digital Camera
16. Stopwatch

Electric Machines

Recent Trends → AI, magnetic field, integrated fiber com. electronics.

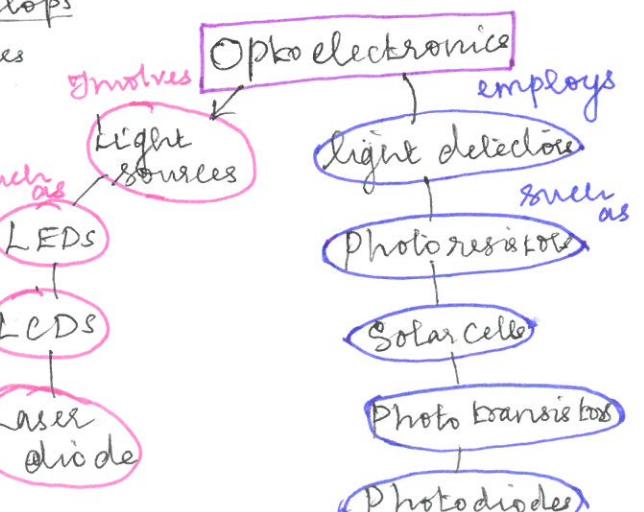- Availability of Solid State devices of large current/voltage handling.
- Cheap micro processors based system for operation and control.
- development of AI tools, expert system for machine design, operation & control, CAD/CAM techniques.



Digital devices

1. LED TV
2. Computer keyboard
3. Digital clock
4. Proximity switch
5. Limit switch
6. Solenoid
7. logic gates
8. Micro processor
9. Random Access memory
10. Solid state drive

All these New Ideas helps young Engineers to develop newer, cheaper, effective Electrical converters and controllers.

* Area - electrical machines.

- Availability of Solid State devices of large current/voltage handling.
- Cheap micro processors based system for operation and control.
- development of AI tools, expert system for machine design, operation & control, CAD/CAM techniques.

1 01 0 1




Engineer to Excel

SIMATS

SCHOOL OF ENGINEERING

Approved by AICTE | IET-UK Accreditation

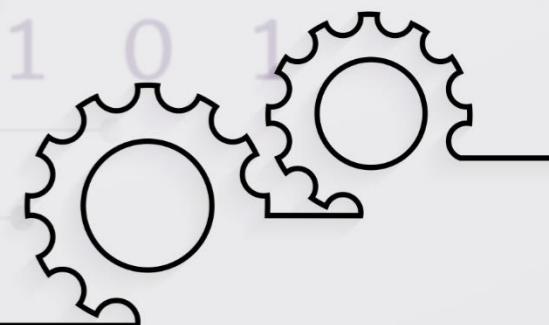

Saveetha Nagar, Thandalam, Chennai - 602 105, TamilNadu, India